

# DC Injection Criteria for PV Systems & Inverter Designs

Karl M.H. LAI (3035273084)

Note:

Some of referred paper are not published. This PowerPoint is ONLY for internal use.

# What matters?

Shayestegan, M. et al (2018), An Overview on Prospects of New Generation Single-Phase Transformerless Inverters for Grid-Connected Photovoltaic (PV) Systems

- IEEE 1547-2018 requires grid-connected inverter system shall not inject DC current **>0.5%** of full rated output current.

## Summary of two prominent standards in grid-connected PV systems

Issue	IEEE1547	IEC61727
Nominal power	30 kW	10 kW
Maximum current THD	5%	5%
Power factor at 50% of rated power	-	0.9
DC current injection	Less than 0.5% (rated output current)	Less than 0.1% (rated output current)
Voltage range (normal operation)	88–110% (97–121 V)	85–110% (196–253 V)
Frequency range (normal operation)	59.3–60.5 Hz	50 ± 1 Hz

Denmark requires HPFI Relay-30mA; Italy, Japan, UK, US, Switzerland requires DC detection device with inverter disable required.


## DC injection limit in different countries

País	Standares	
USA	IEEE 929-2000	The PV system should not inject current >0.5% of rated power inverter ground output current into the AC interface under either normal or abnormal operation conditions.
Japan	Technical guideline for the grid interconnection of dispersed power generating systems	DC injection detection device with inverter disable is required for transformerless inverters. Maximum allowable DC current level is 1% of inverter rated current.
Germany	DIN VDE 126	DC sensitive residual current device required. Disconnection required if a step of 30 mA or larger within 1 s occurs, or the continuous residual current exceeds 60 mA per kVA or inverter rated power. DC injection detection device with inverter disconnection is required for transformerless inverters. Detection threshold is 1 A.
Spain	RD 1663/2000	No limits.
Australia	AS 3300	DC current not to exceed 5 mA. Guidance form AS3300 50 Hz transformer interface between DC and AC preferred transformerless inverters must have DC injection detection device.
The United Kingdom	G83 England G77	Use of an isolation transformer is recommended. A DC injection detection device with inverter disable is required for transformerless inverters, the maximum DC current limit is 5 mA.

# What's matter?

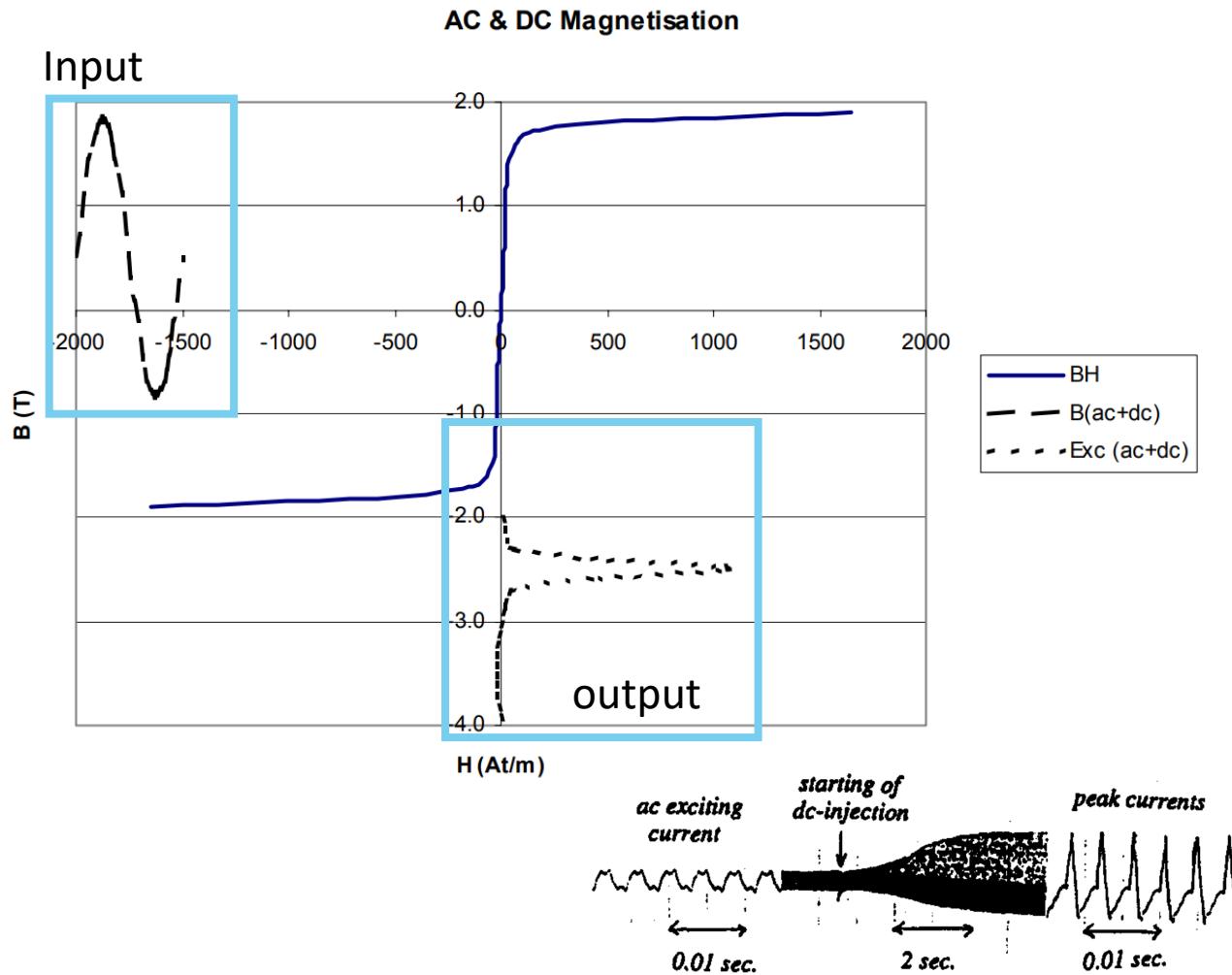- Problems of DC Injection:
  - shift the transformer operation point, transformer saturation
  - waveform distortion → pulsating torque/overheat in machine
  - electrochemical corrosion for underground cable
  - malfunction of protection equipment



Gubia, E. et al. (2007), Ground currents in single-phase transformerless photovoltaic systems, Prog. Photovoltaics  
 Akhmad, K. et al. (1997), AC side harmonics and phenomena accompanying DC-injection of utility-interactive PV system



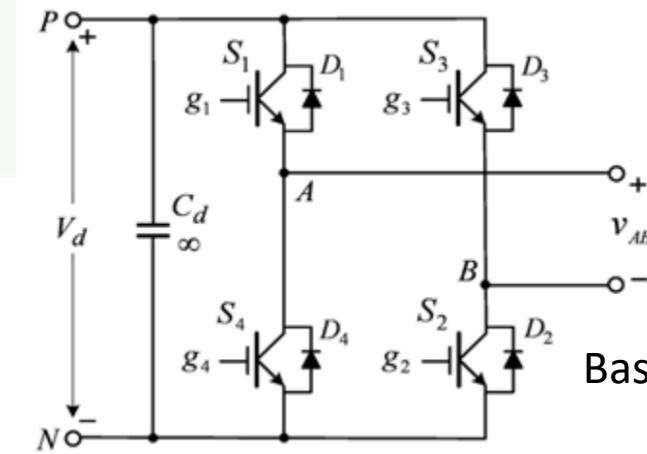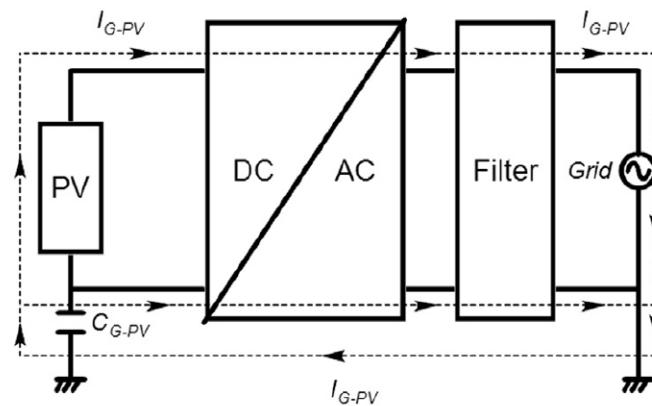
# What's matter?

- DC Injection is from:
  - detection error (delay, A/D, current sensors)
  - tolerance of power switching devices
  - asymmetry of PWM gating driving pulses
  - ground current flowing between inverter output and DC stage (due to stray capacitance between PV panels and ground)
  - ON-state forward saturation voltage & ON-state resistance (switch)

Ground Current Leakage in Transformerless PV Systems



Basic Inverter

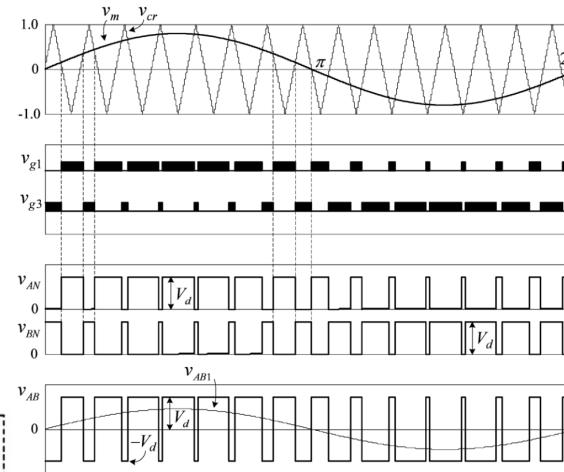


Bipolar Switching

$$v_{cm} = \frac{v_{AN} + v_{BN}}{2} = \text{const. for Bipolar Switching}$$

(but fluctuating for Unipolar)

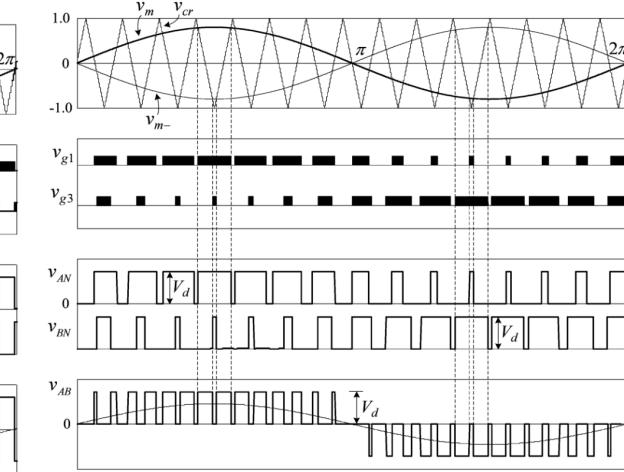Bipolar will lead to voltage swing, high switching loss







Unipolar Switching
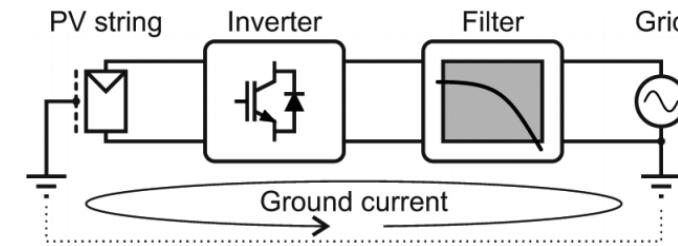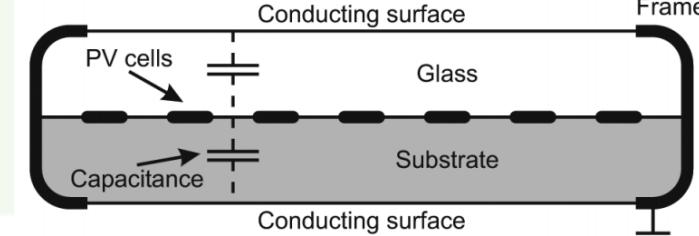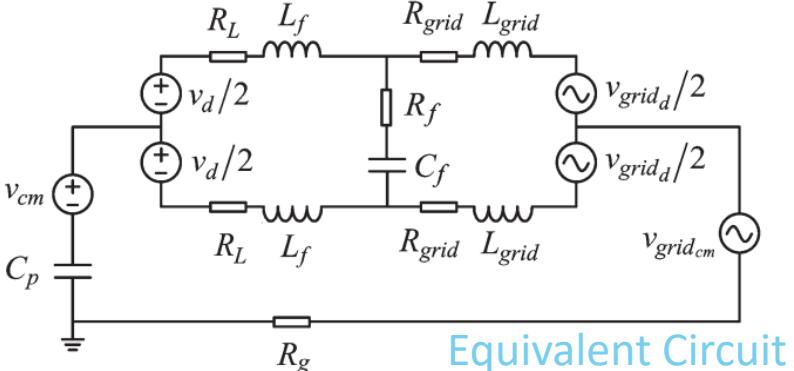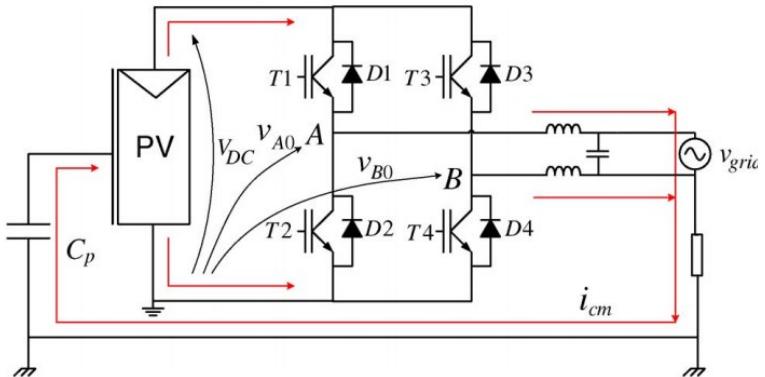
# What's matter?

Barater D, et al (2014) Active Common Mode Filter for Ground Leakage Current Reduction in Grid Connected PV Converters Operating with Arbitrary Power Factor  
 Lopez O, et al (2010) Eliminating Ground Current in a Transformerless Photovoltaic Application

- **Ground Current Injection (Common Mode)**



$$v_{cm} = \frac{v_{A0} + v_{B0}}{2} \quad i = C \frac{dv_{cm}}{dt}$$



Ground current depends on the **change** of common mode voltage (voltage at the output of full bridge inverter)

Ground current appears due to **unipolar switching** (vs bipolar switching)


Transformless Design should take care of **resonance** due to ground current loop

Ground current can be eliminated with stabilizing  $v_{CM}$  with **reference to grid voltage**

**Safety** and **noise** are concerns.

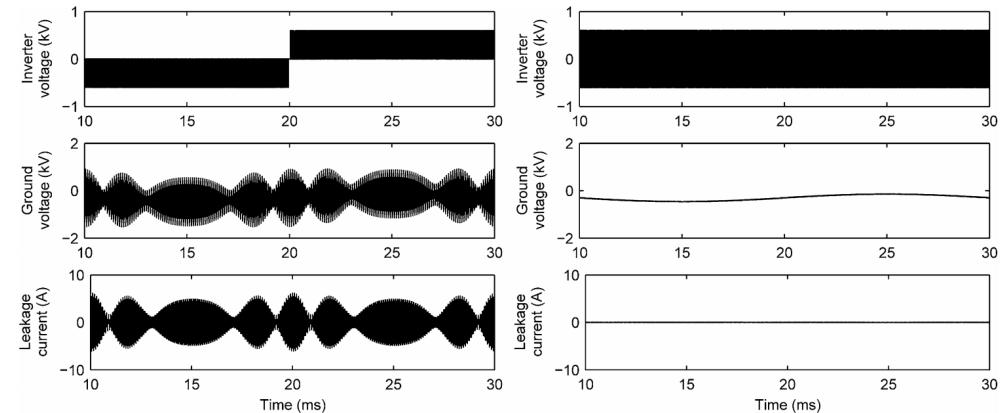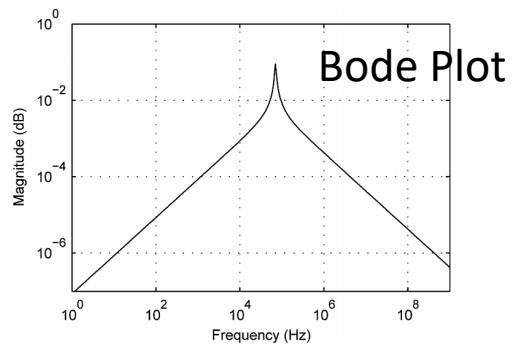


# Common Mode in a Nutshell

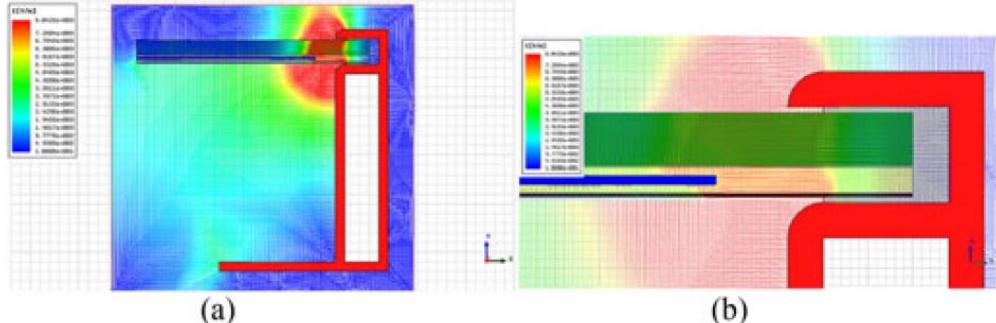

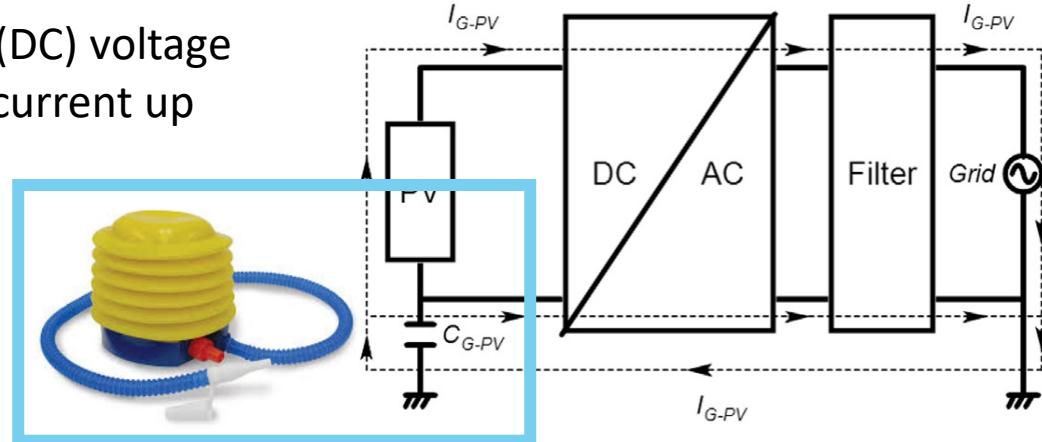(a) E-field around PV and metal frame

Parasitic Capacitance ranges **from  $\mu\text{F}$  to  $\text{nF}$** , depending on **ground nature, weather, topology, module structure**.




Change of (DC) voltage will pump current up



Equivalent Circuit for CMV:

$$V_{tCM} = V_{CM} + \frac{V_{DM}}{2} \frac{L_B - L_A}{L_A + L_B}$$

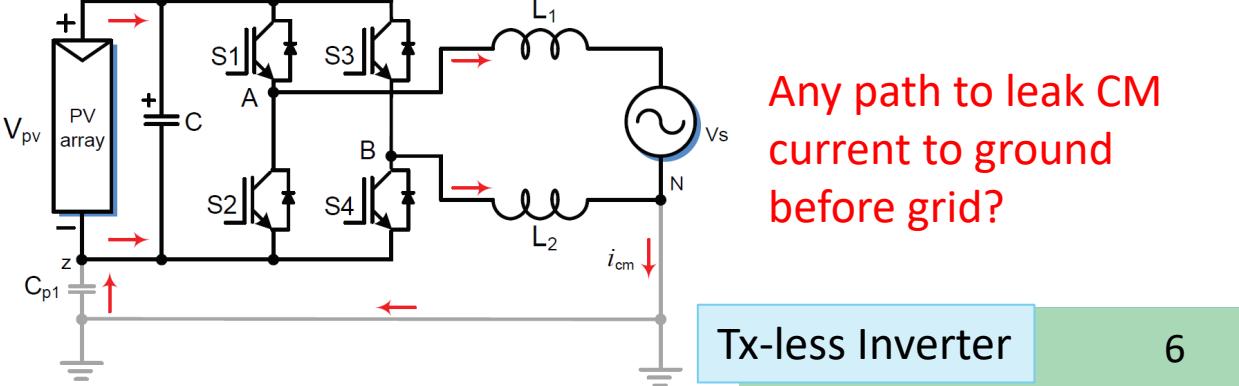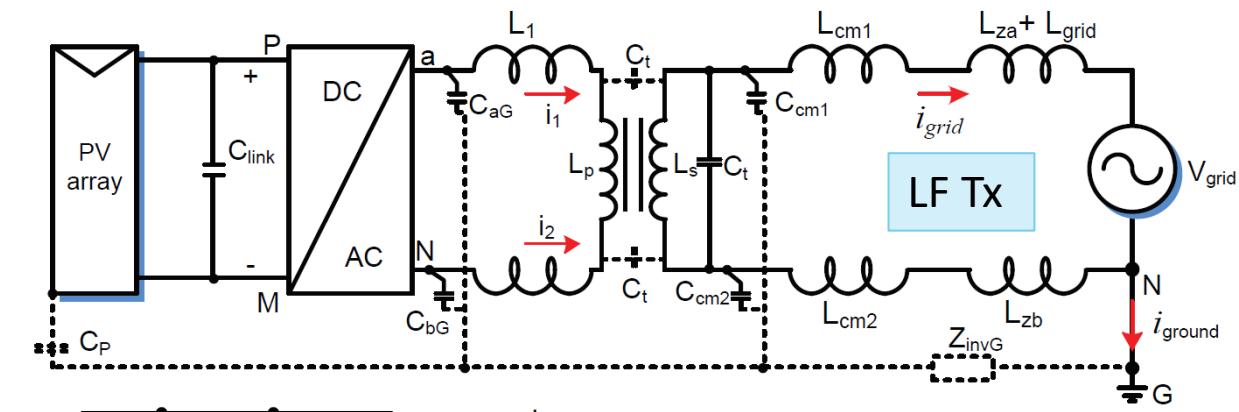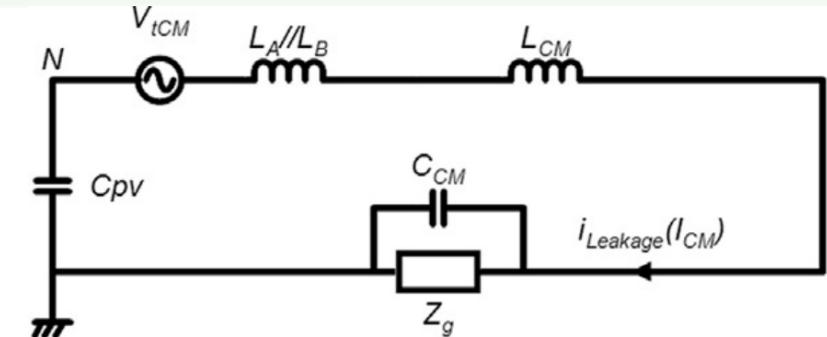
$$V_{CM} = \frac{1}{2}(V_{AN} + V_{BN})$$



Any path to leak CM current to ground before grid?
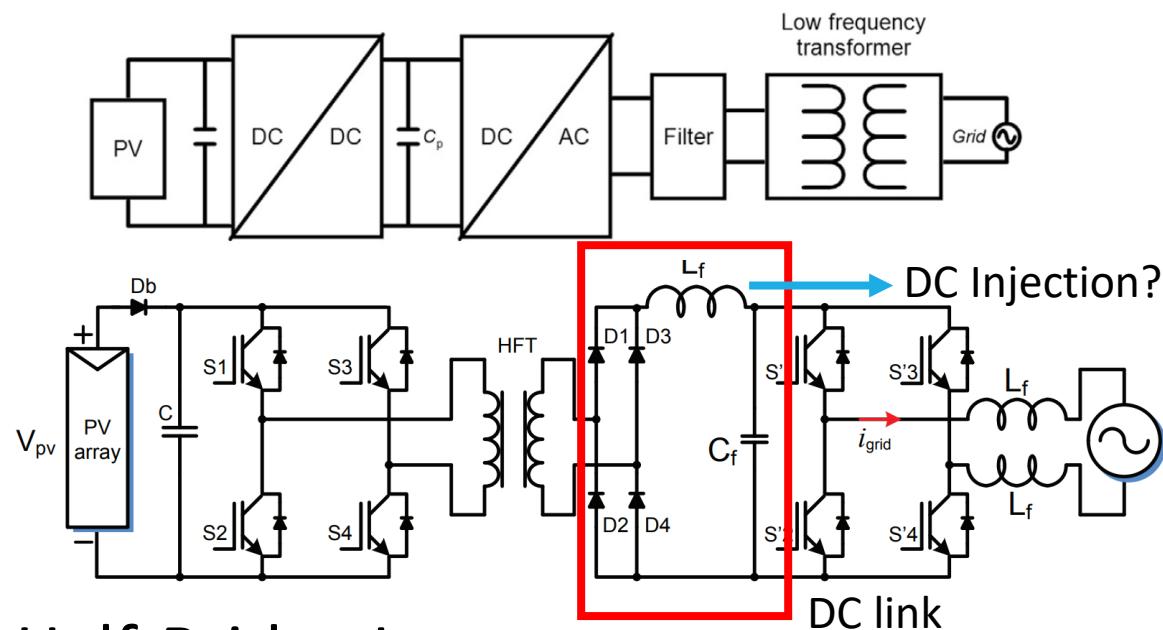
# Common Solutions

- Isolation Transformer  
(or High Frequency Transformer)





- Half-Bridge Inverter

Prevent current flow but requires twice DC bus voltage and stronger switches and capacitor

Berba, F. et al. (2014), A new approach of prevention of DC Current Component in Transformerless Grid-Connected PV Inverter Application

- Blocking capacitor

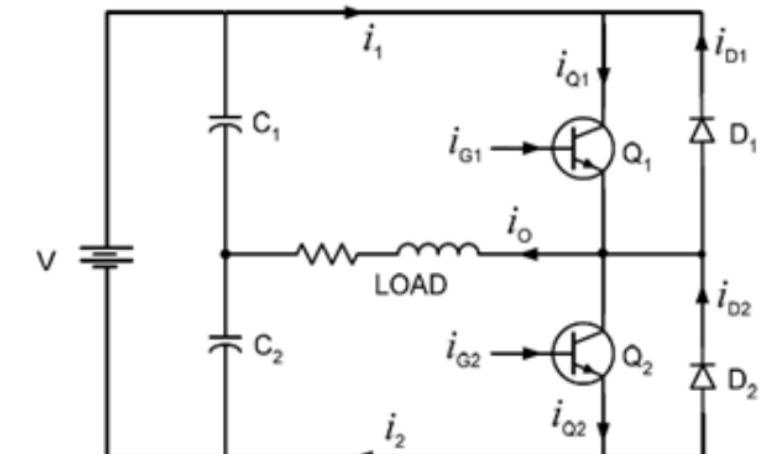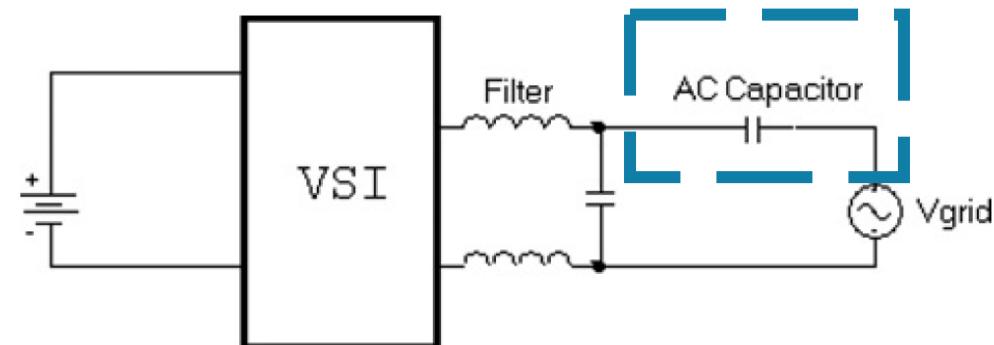

Salas V. et al. (2006), DC Current Injection into the Network from PV Grid Inverters  
 Medina A. et al. (2014), DC Current Injection into the Network from Transformerless and LF Transformer Photovoltaic Inverter

# Amount of DC

Past Data:

Laptop: 0.04A DC (7.7% of rated)

Desktop: 0.03A DC (11.2% of rated)

Lighting: 0.34A DC (0.53% of rated)

**Some may have DC more than PV's**

DC comes from Fourier Series:



$$f(t) = a_0 + \sum a_n \cos nwt + b_n \sin nwt$$

where  $a_0 = \frac{1}{T} \int_t^{t+T} f(t) dt$  (average)

which is the DC component.


Even there is LF transformer,  
 There can be DC. (gate triggering)

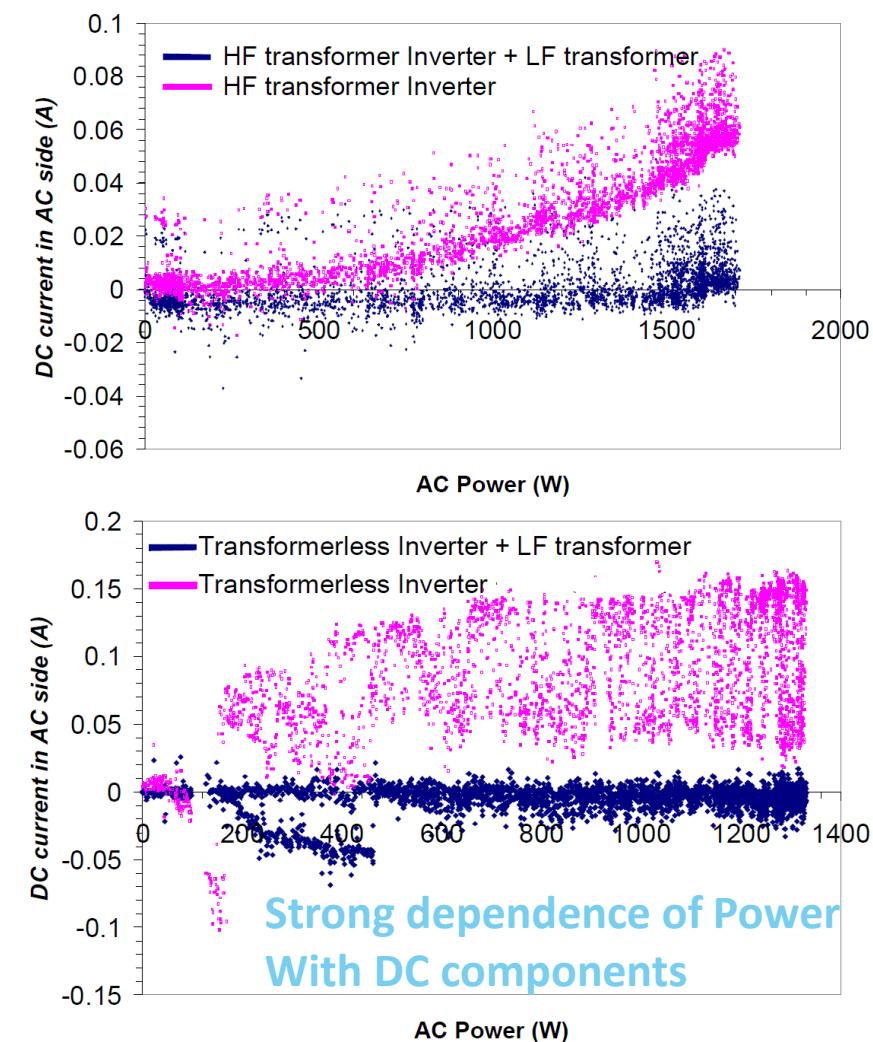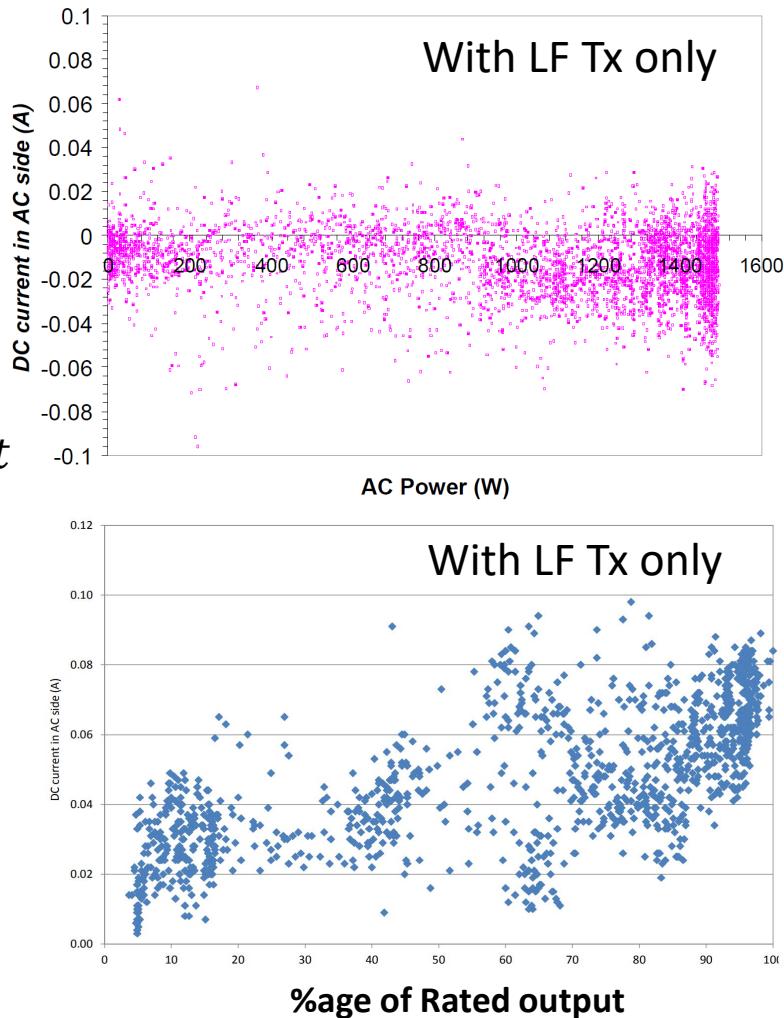Comparing DC component,  
 Transformerless > HF Tx > LF Tx



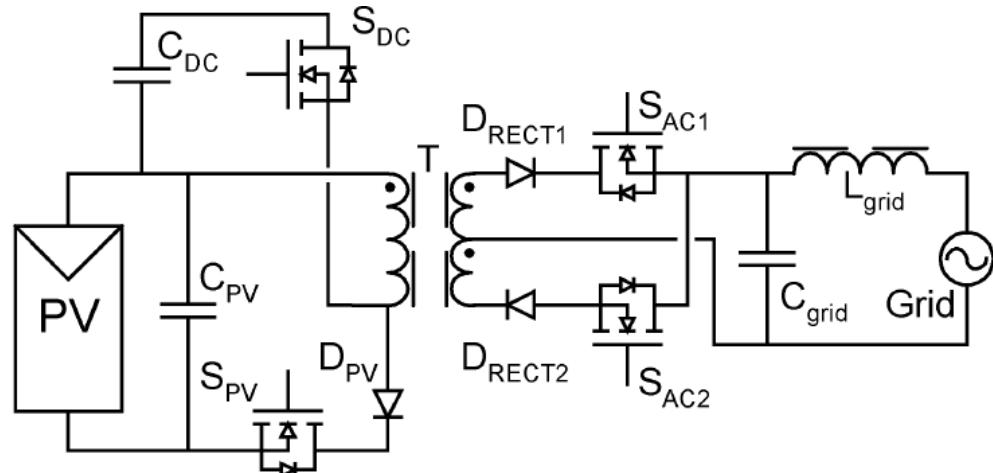
# Common Inverter Topology to be used


Kjaer S. B. et al (2005), A Review of Single Phase Grid Connected Inverter for PV Module



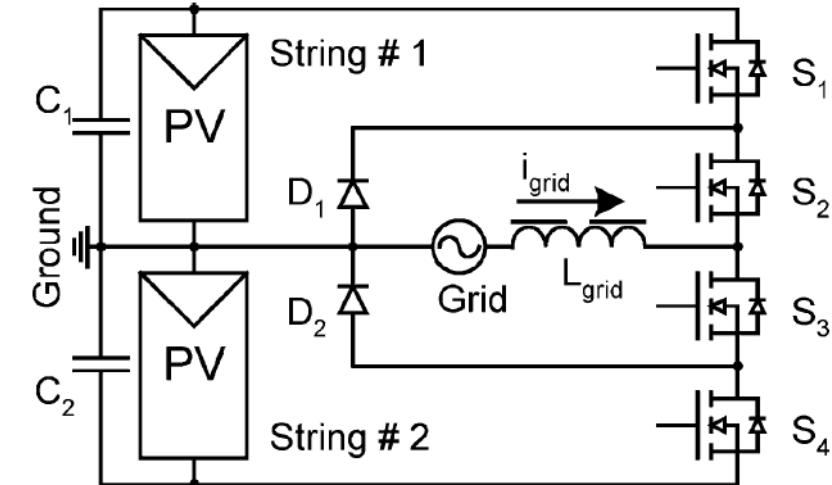Flyback inverter with high power decoupling



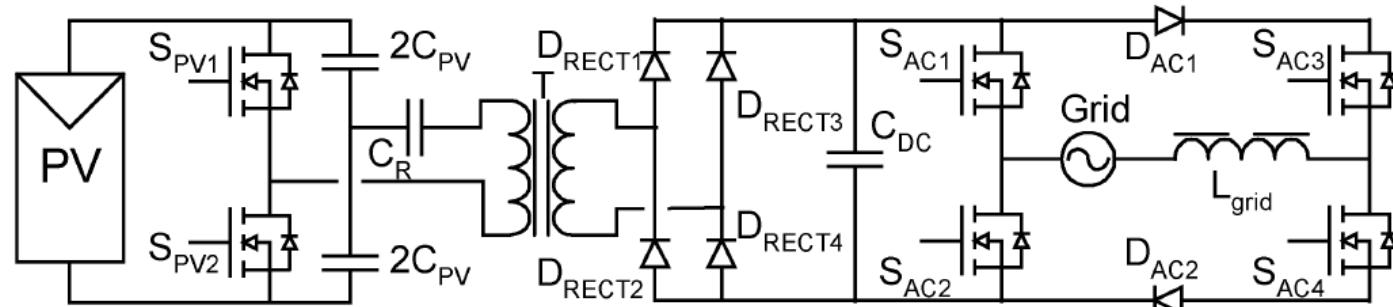Half-bridge diode clamped three level inverter




Series resonant converter with bang-bang dc-ac inverter

Flyback applies transformer, series cap and diode offset to mitigate DC  
Series Resonant Converter has high step-up ratio and series cap to mitigate DC  
Half bridge converter stops DC flowing from ground

# Latest Solution

Guo X. et al. (2008), DC Injection Control for Grid-Connected Inverters Based on Virtual Capacitor Concept

- Virtual Capacitor

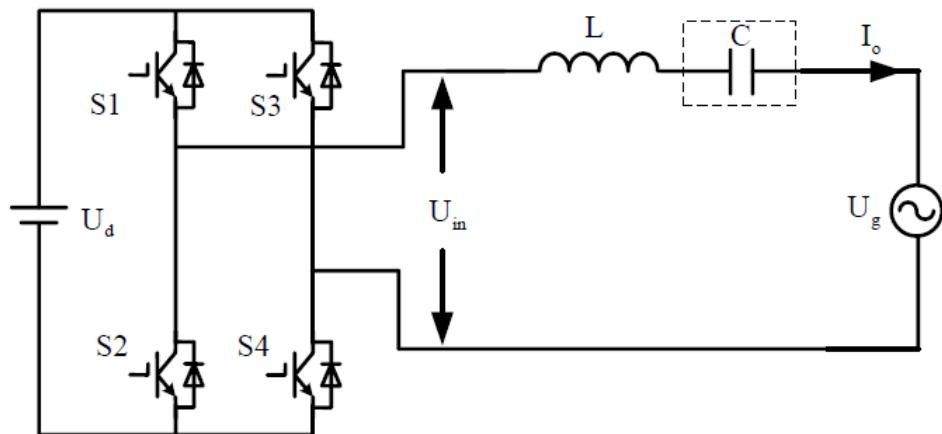

$$G(s) = k_p + \frac{k_i s}{s^2 + \omega^2}$$

$$U_{in} = L \frac{di_o}{dt} + \frac{1}{C} \int i_o dt - U_g$$



$$\frac{i_o(s)}{U_{in}(s) - U_g(s)} = \frac{Cs}{LCs^2 + RCs + 1}$$

$$I_o(s) = \frac{KG(s)}{Ls + R + KG(s) + \frac{1}{Cs}} I_{ref}(s) - \frac{1}{Ls + R + KG(s) + \frac{1}{Cs}} U_{grid}(s)$$

Assume:

- DC Bus voltage is constant
- Switching Freq is high enough
- Inverter output does not saturate

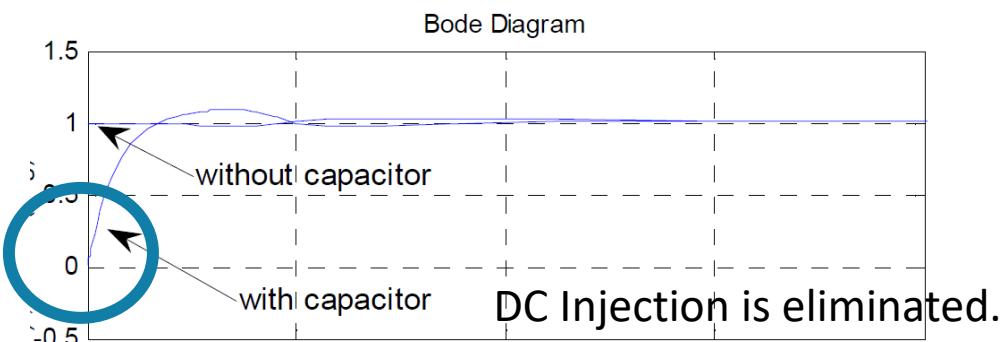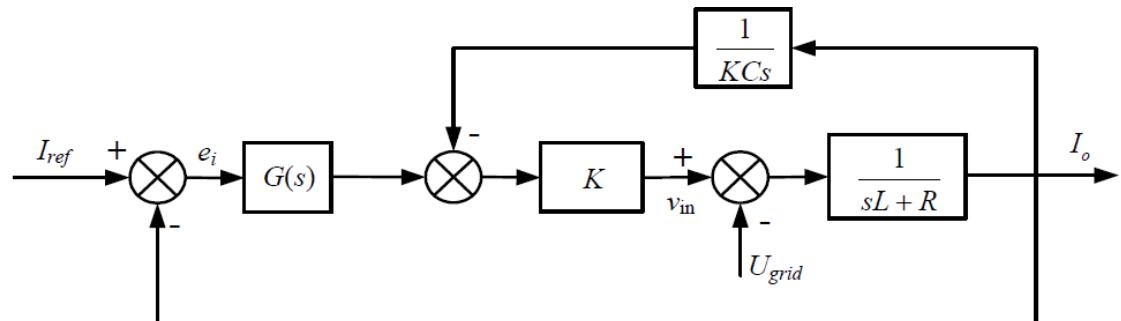
To avoid using large and expensive capacitor, we include capacitor effect in the output of inverter.



# Latest Solution

Blewitt W.M. et al. (2008), Approach to low-cost prevention of DC Injection in Transformerless Grid Connected Inverters  
 Armstrong M, et al. (2006), Auto-Calibration DC Link Current Sensing Technique for Transformerless, Grid Connected, H-Bridge Inverter Systems  
 Butler J.W. & Concordia C. (1937), Series Capacitor Application Problem

- DC offsets and autocalibration

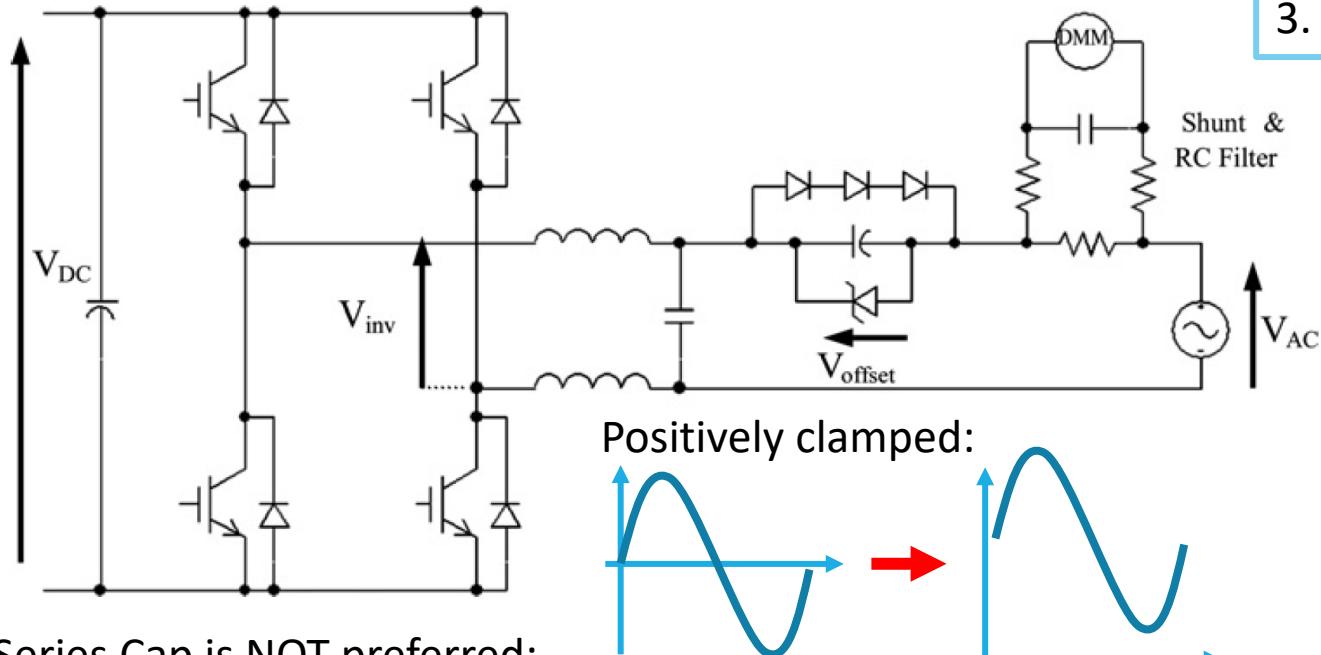

Series Cap is NOT preferred:

1. Overshoot for flickers and voltage rise
2. Distorted and large Tx exciting current  $\rightarrow$  saturation
3. Hunting of synchronous machine/ self-excitation of induction motor


1. Electrolytic Capacitor with offset voltage is used
2. Diode clamp to protect the cap from reverse polarity
3. Shunt/ RC filter install to obtain DC current value

To tune  $V_{inv}$  to control  $I_{out}$ :

$$V_{inv} = V_{ac} + V_L$$

$$V_L = j\omega L I_{out}$$
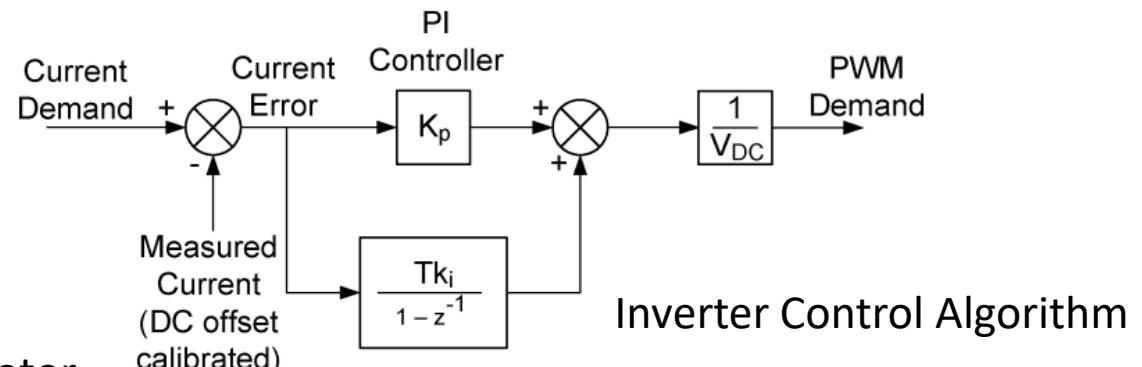
$$I_{out} = \frac{V_{inv} - V_{ac}}{j\omega L}$$



Inverter Control Algorithm

# Latest Solution

He G.F. et al. (2015), A novel control strategy of suppressing DC current injection to the grid for single-phase PV inverter  
Li, S. et al, (2014), Suppressing Method for Photovoltaic Power Station DC Component Injection

- DC Suppression Loop (with PI controller)

Mainly focused on differential mode.





### Feedback gain with LPF and Diff. Amplifier:

$$G_{\text{dc}}(s) = \frac{2}{\left(1 + \frac{s}{2\pi f_{LP}}\right)^2}$$

Assigning  $K_p$  and  $K_i$ , with turn point 5Hz:

$$\left\{ \begin{array}{l} \frac{K_{id}}{2\pi K_{pd}} = 5 \\ \left| G_{dc\_offset}(s) \cdot \frac{(K_{pd}s + K_{id})}{s} \right|_{s=2\pi} = 1 \end{array} \right.$$


## Sampling circuit:

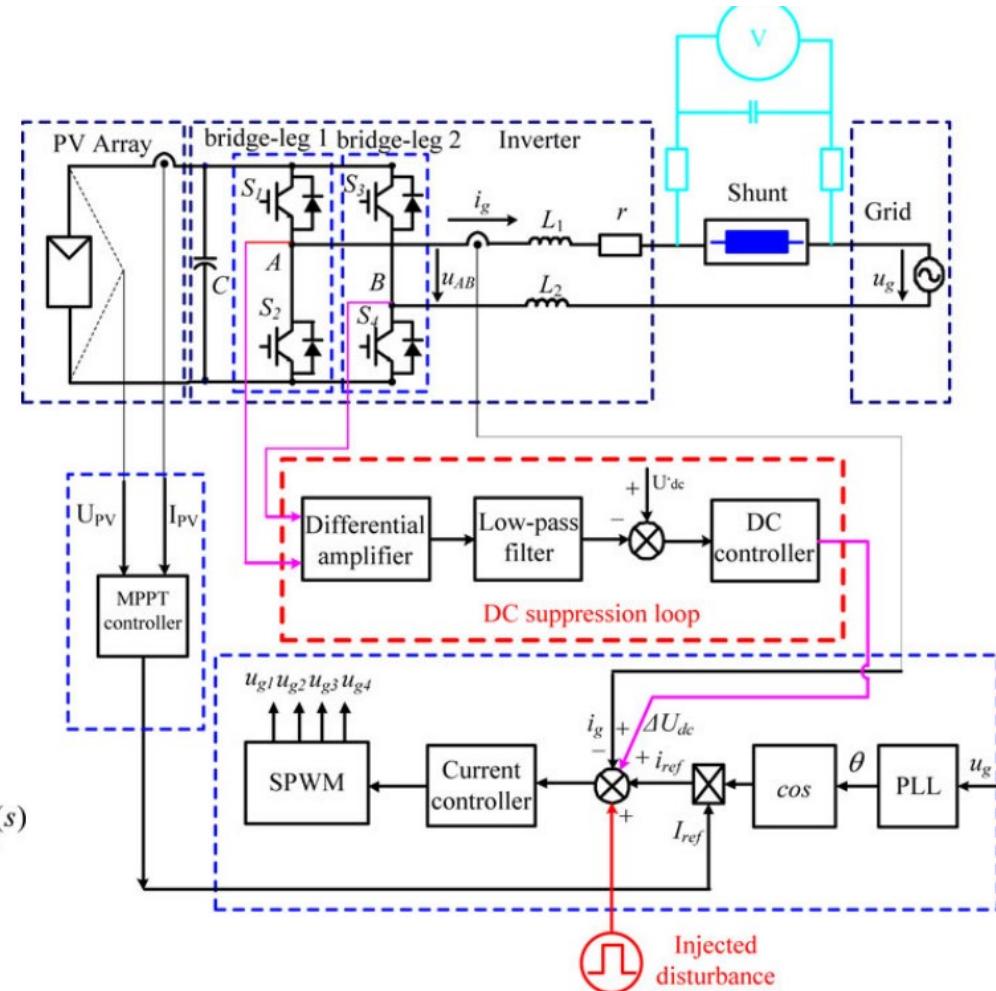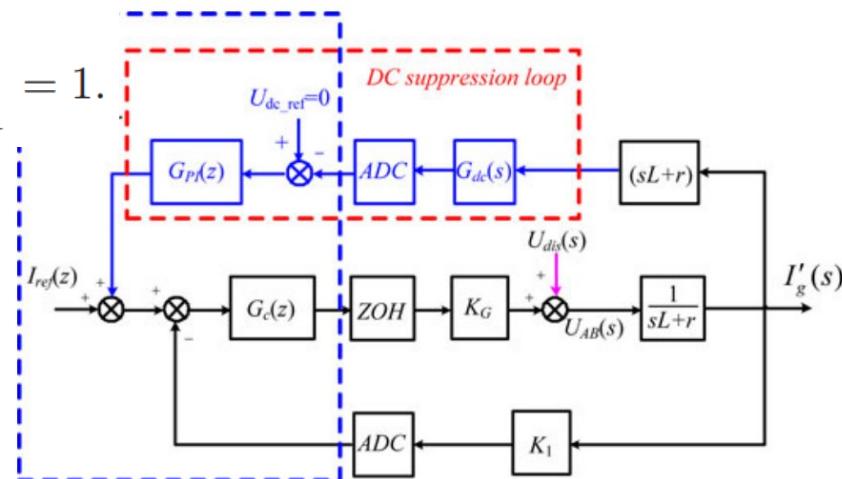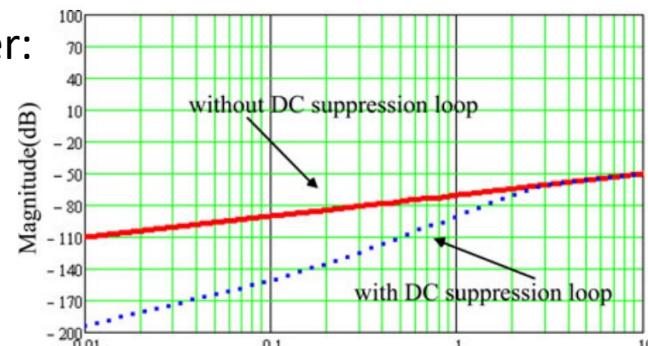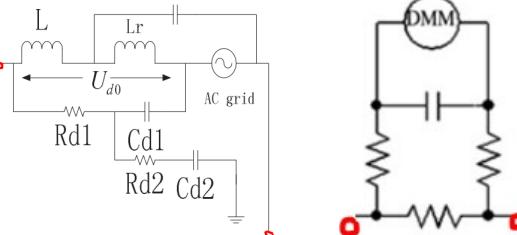

# Latest Solution

Chen, M. et al. (2018), A Novel DC Current Injection Suppression Method for Three-phase Grid Connected Inverter Without Isolation Transformer

- Synchronous Frame Control

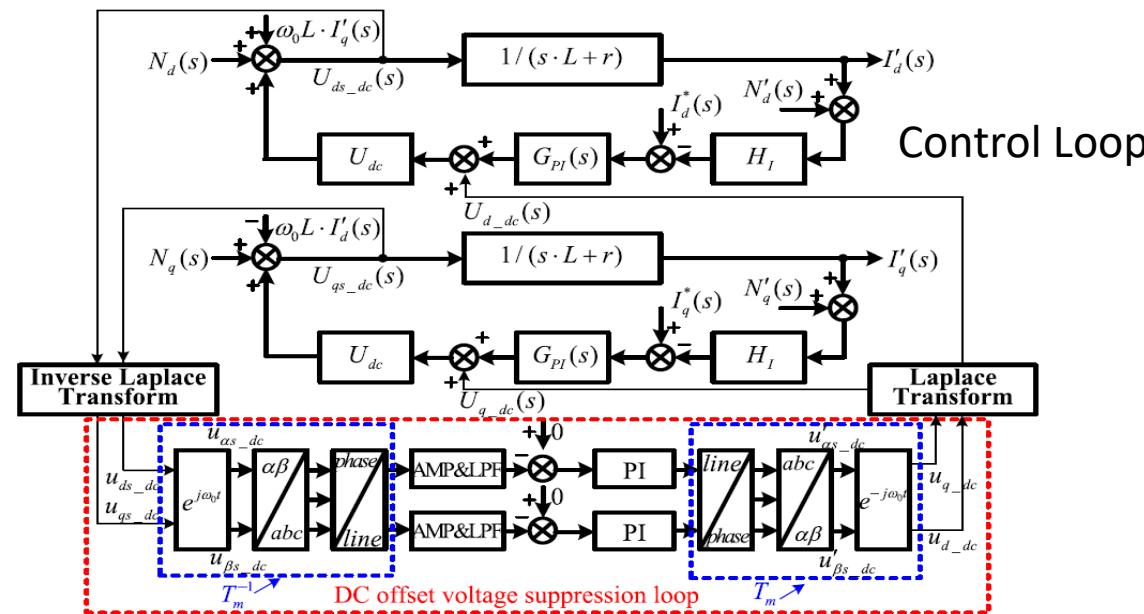


Mainly focus on Differential Mode Current

$e$  = detection error

$R$  = sampling circuit error

$$\Delta I_A = \pm \left( e\% + R\% + \frac{1+M}{2^N} \right) \times I_{p-p}$$


$(1+M)/2^N$  = ADC resolution error

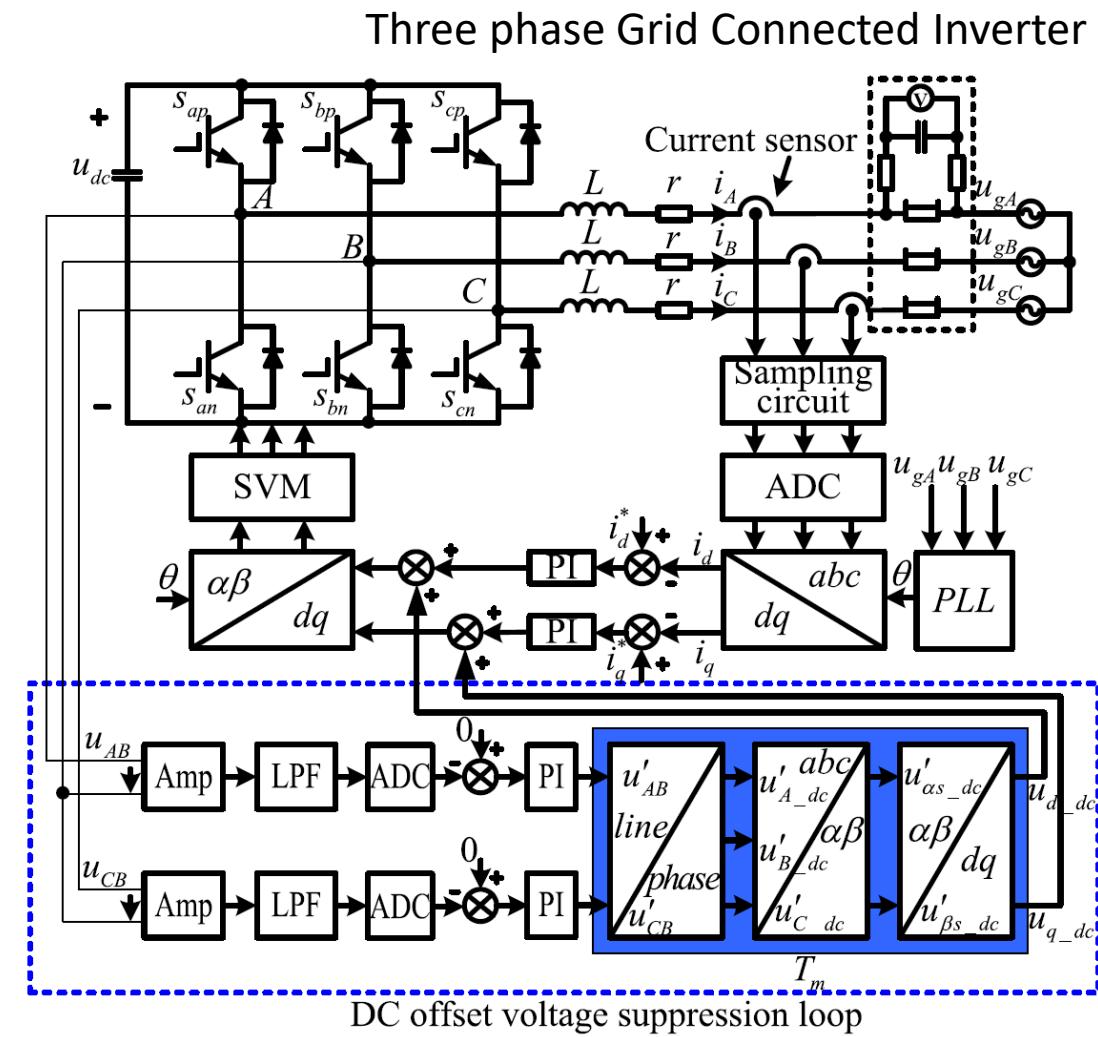

# Latest Solution

Wang, B. et al (2010), Real-time DC Injection Measurement Technique for Transformerless PV Systems

- Better Measurement Technique

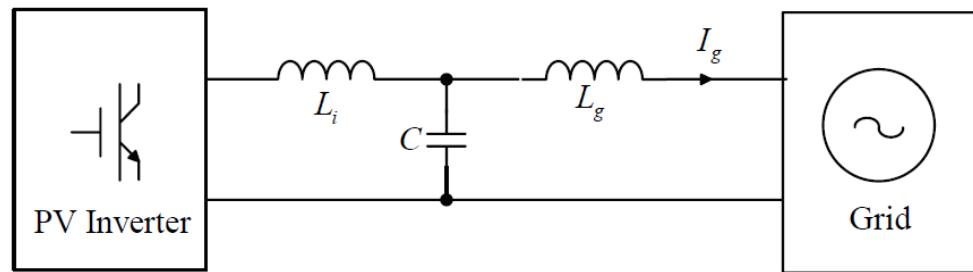

$$\begin{aligned}
 I_c(t) &= \frac{1}{T} \int_{t_0}^{t_0+T} I_g(t) dt \\
 &= \frac{1}{T} \int_{t_0}^{t_0+T} [I_0 + \sum_{n=1,2,3,\dots} I_n \sin(2\pi n f_1 t + \varphi_n)] dt \\
 &= I_0 + \sum_{n=1,2,3,\dots} \left[ \frac{f_0}{\pi n f_1} \sin\left(\frac{\pi n f_1}{f_0}\right) \times I_n \sin\left(2\pi n f_1 t_0 + \varphi_n + \frac{\pi n f_1}{f_0}\right) \right]
 \end{aligned}$$

Error Amplitude

When PV freq ( $f_0$ ) is different from grid freq ( $f_1$ )

$$\begin{aligned}
 I_g(t) &= I_{dc} + I_{ac} = I_0 + \sum_{n=1,2,3,\dots} I_n \sin(2\pi n f_1 t + \varphi_n) \\
 I_b(t) &= \frac{1}{T} \int_{t_0}^{t_0+T} I_0 dt = I_0 \\
 I_c(t) &= \frac{1}{T} \int_{t_0}^{t_0+T} I_g(t) dt \\
 &= \frac{1}{T} \int_{t_0}^{t_0+T} [I_0 + \sum_{n=1,2,3,\dots} I_n \sin(2\pi n f_1 t + \varphi_n)] dt \\
 &= I_0
 \end{aligned}$$

Proposed Measurement  
 $T = 1/f_1$

$$\begin{aligned}
 I_{cc}(t) &= \frac{1}{T^2} \int_{t_0}^{t_0+T} I_c(t) dt \\
 &= \frac{1}{T^2} \int_{t_0}^{t_0+T} \left[ \int_{t_0}^{t_0+T} I_0 + \sum_{n=1,2,3,\dots} I_n \sin(2\pi n f_1 t + \varphi_n) dt \right] dt \\
 &= I_0 + \sum_{n=1,2,3,\dots} \left[ \frac{f_0}{\pi n f_1} \sin\left(\frac{\pi n f_1}{f_0}\right) \right]^2 \times I_n \sin\left(2\pi n f_1 t_0 + \varphi_n + \frac{2\pi n f_1}{f_0}\right)
 \end{aligned}$$



Double Integration solves the problem

# Latest Solution

Hasanzadeh A. (2012), Reduced Switch NPC-based Transfromerless PV Inverter by Developed Switching Pattern

- Conergy Neutral Point Clamped (NPC) topology

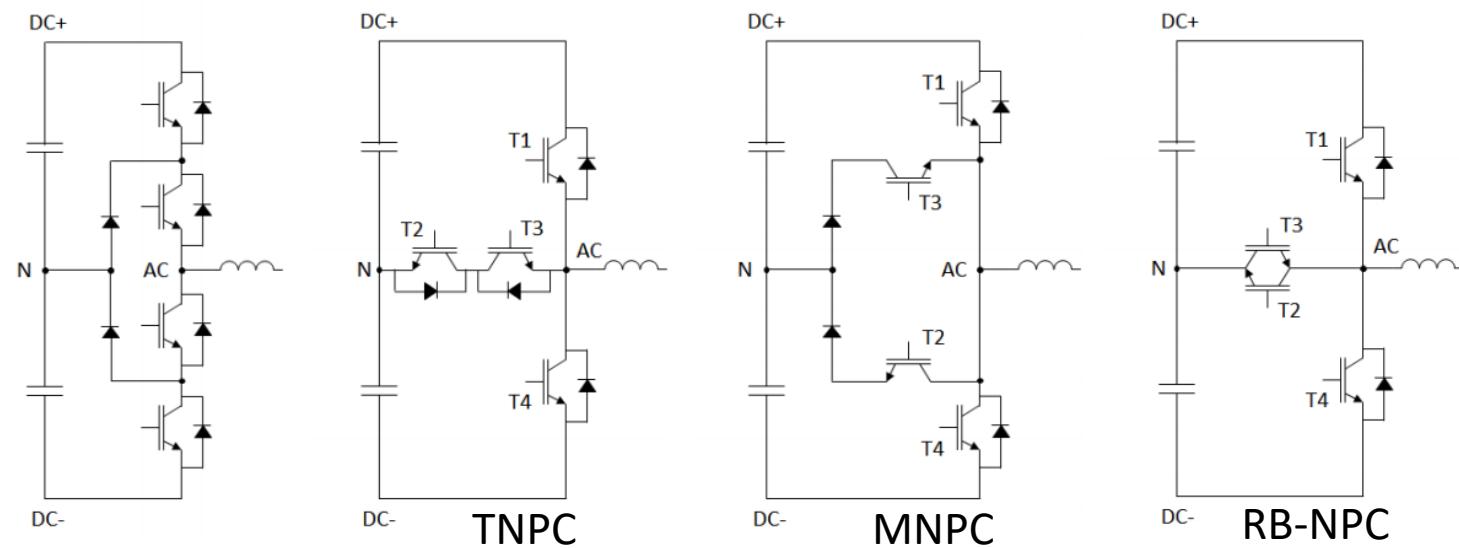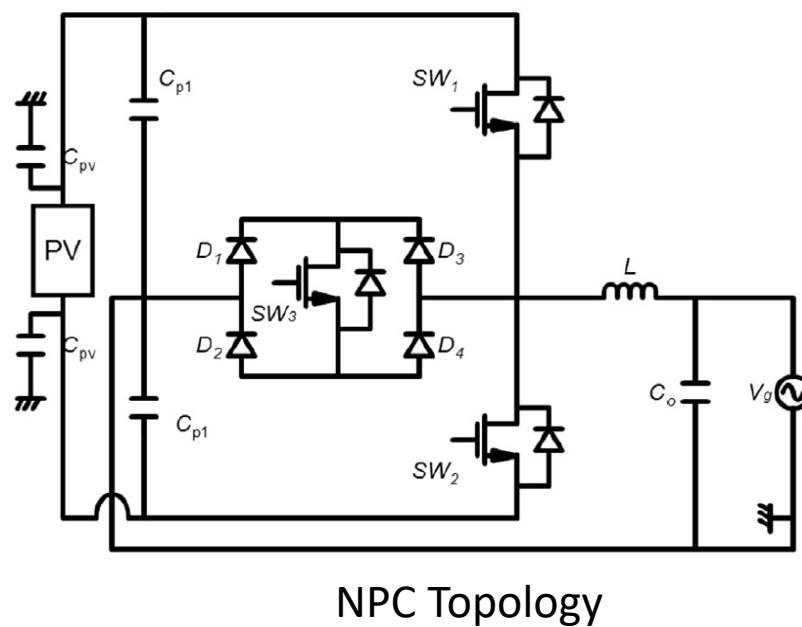
Half-bridge (HB) requires **higher rating switches** and produces distorted output current with high EMI and switching loss.



Half-bridge can inhibit **leakage current** through parasitic capacitance of the module  
→ we have NPC topology

# Latest Solution

- H5 Topology

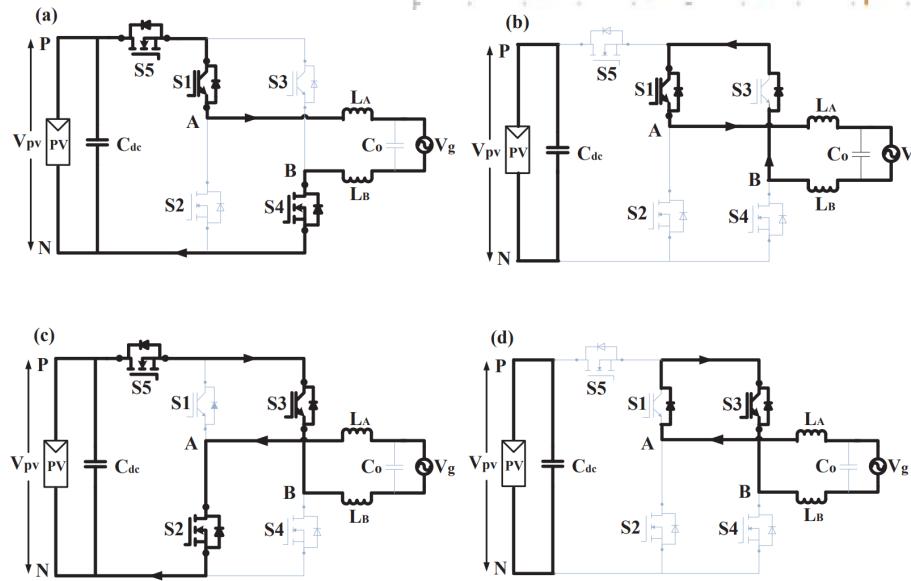


**Constant common mode voltage during switching**

Slope of  $V_{cm}$  depends on **Junction Capacitance**  
especially in **free-wheeling mode**

$I_{cm}$  (25mA/div)

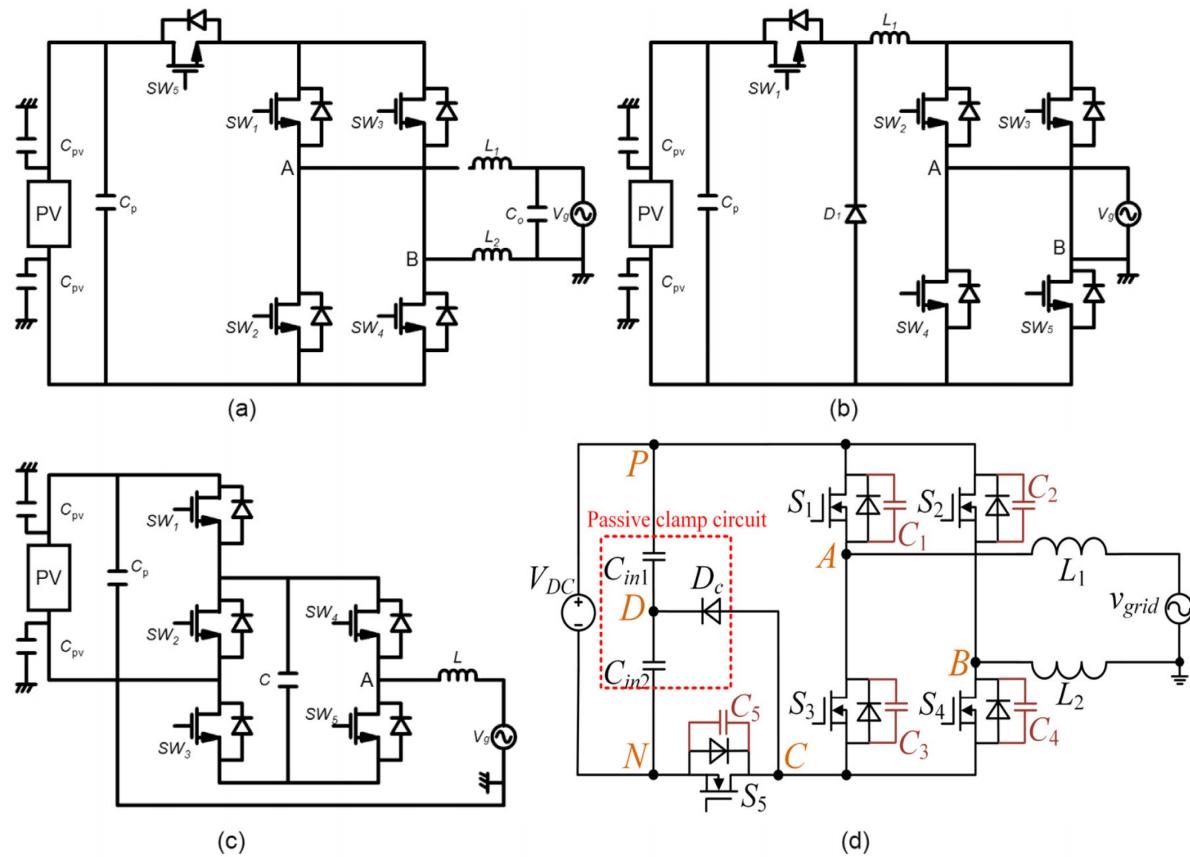Islam, M. et al. (2014), An Improved Transformerless Grid Connected Photovoltaic Inverter with Common Mode Leakage Current Elimination  
Li, H. et al. (2018), An Improved H5 Topology with Low Common Mode Current for Transformerless PV Grid-Connected Inverter





Different Types of H5 Inverter

# Latest Solution


Hasanzadeh A. (2012), Reduced Switch NPC-based Transfromerless PV Inverter by Developed Switching Pattern

- HERIC Topology:

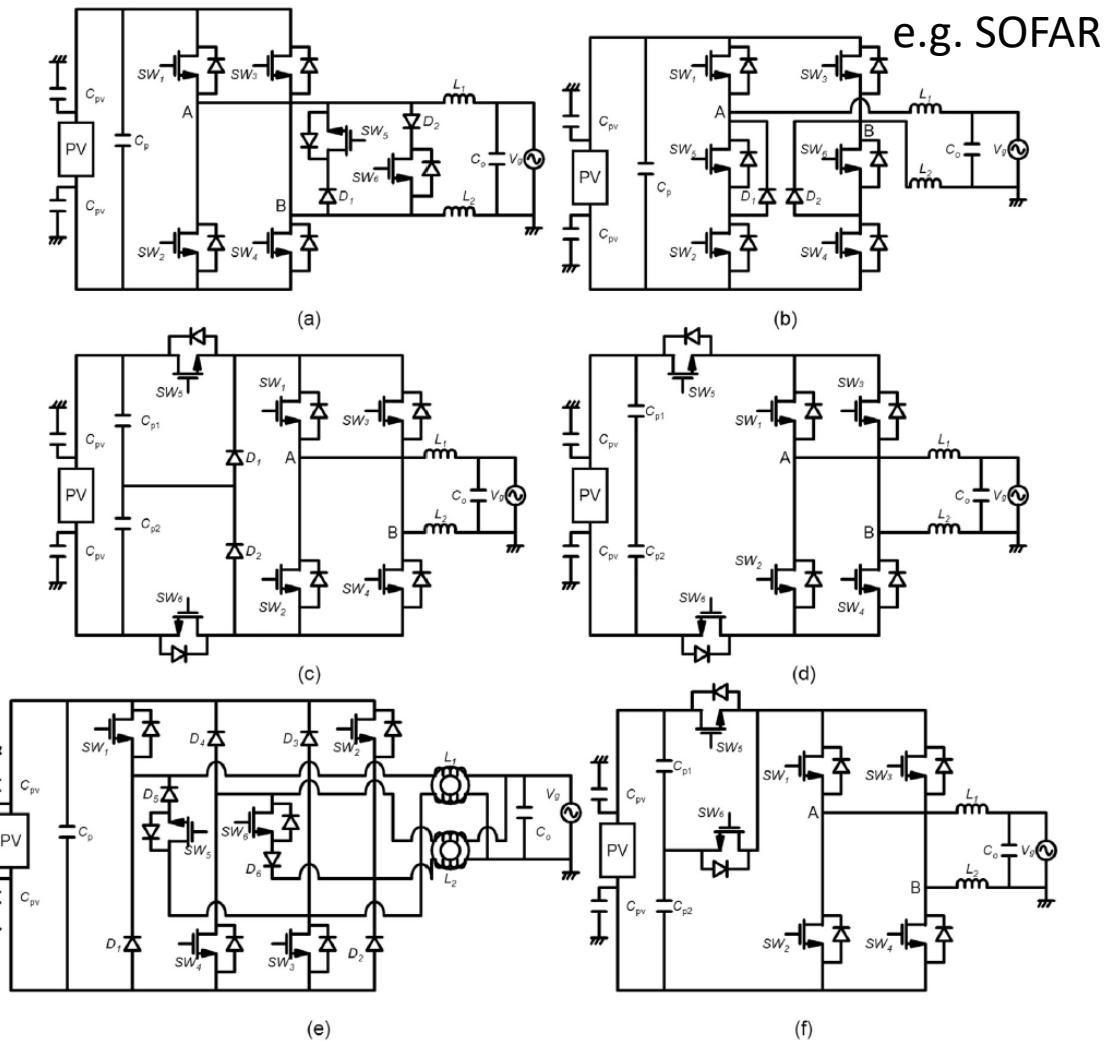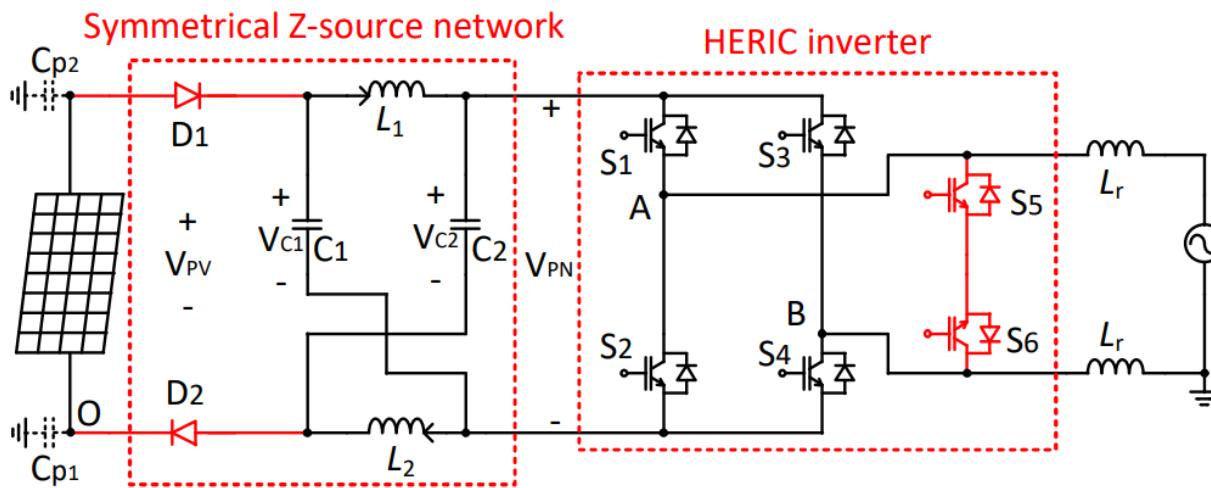- Common in commercial inverter (e.g. Sunway)
- Avoid occurrence of leakage current
- Three level output voltage
- High efficiency & Unipolar PWM




# HERIC switching

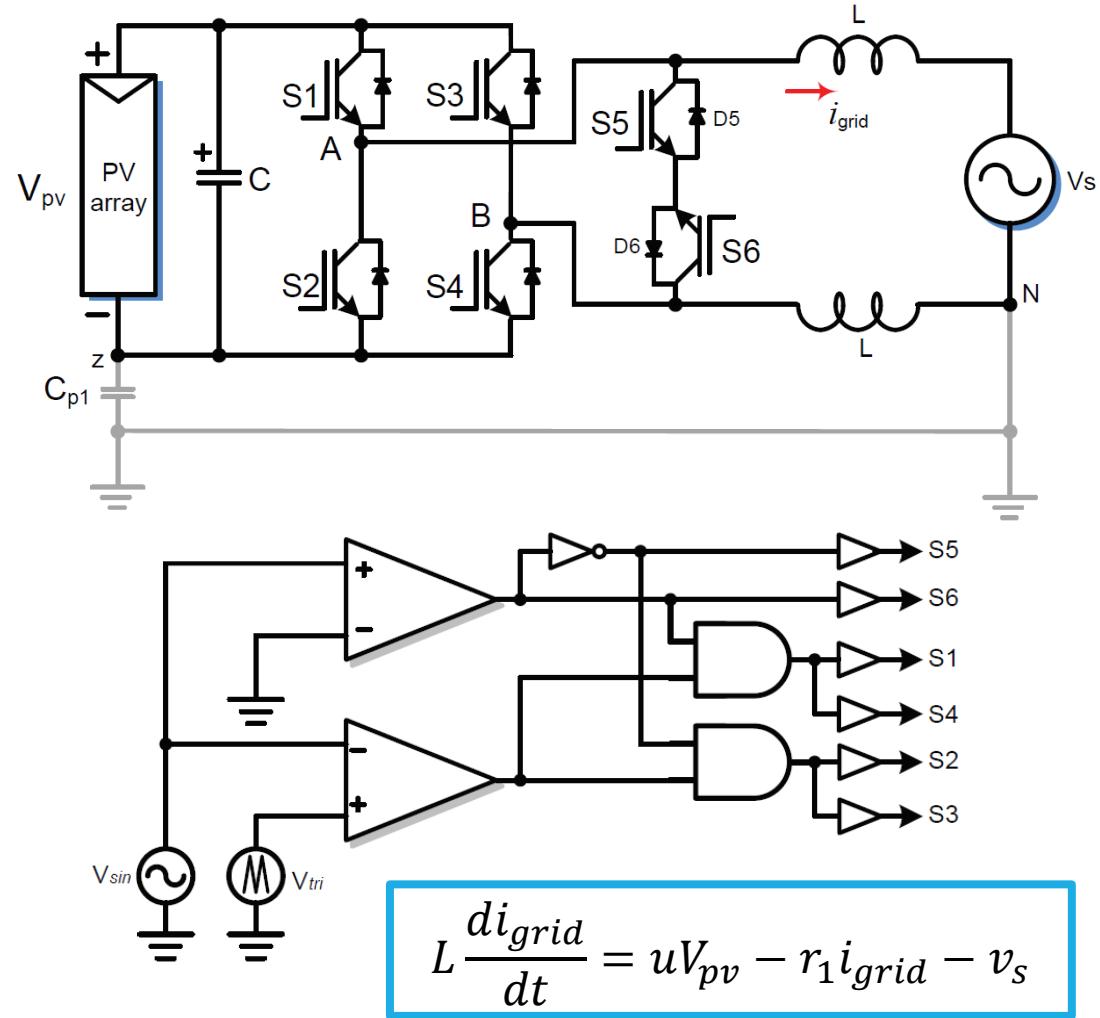

Constant voltage in CM

Switching Topology

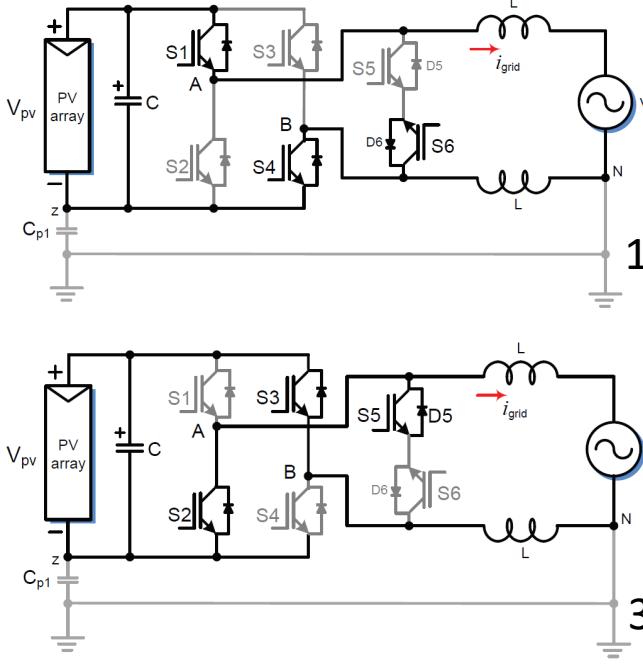

Positive:


$$V_{cm} = \frac{V_{AZ} + V_{BZ}}{2} = \frac{V_{DC} + 0}{2} = \frac{V_{DC}}{2}$$

Zero:

$$V_{cm} = \frac{V_{AZ} + V_{BZ}}{2} = \frac{\frac{V_{DC}}{2} + \frac{V_{DC}}{2}}{2} = \frac{V_{DC}}{2}$$


Negative:
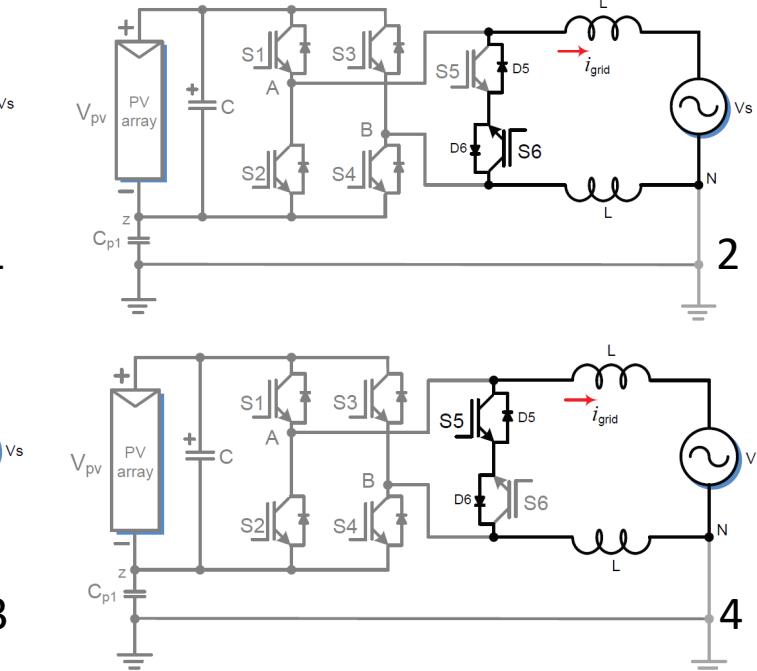
$$V_{cm} = \frac{V_{AZ} + V_{BZ}}{2} = \frac{0 + V_{DC}}{2} = \frac{V_{DC}}{2}$$



# Latest Solution

- Passive Filter (e.g. CM Choke)

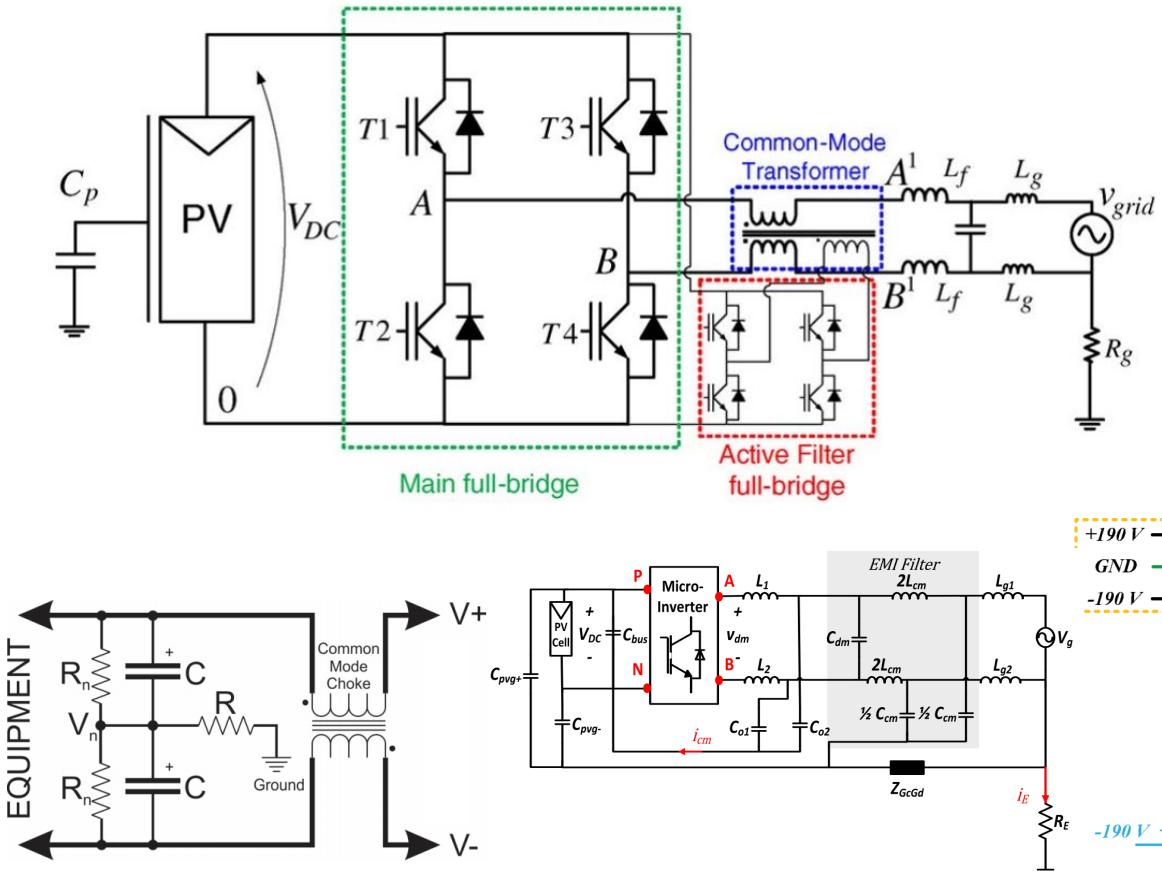


Doerry, N & Amy J.V. (2017), MVDC Grounding and Common Mode Current Control  
 Chen, F. et al. (2018), A Bidirectional High-Efficiency Transformerless Converter with Common Mode Decoupling for the Interconnection of AC and DC Grid  
 Bortis, D. et al (2016), np-Pareto Optimization and Comparative Evaluation of Inverter Concepts considered for the Google Little Box Challenge

To prevent **resonant** and **DC injection**, L-C filter/ chokes should be properly sized.

Resistor is added in to increase **high freq. Impedance**

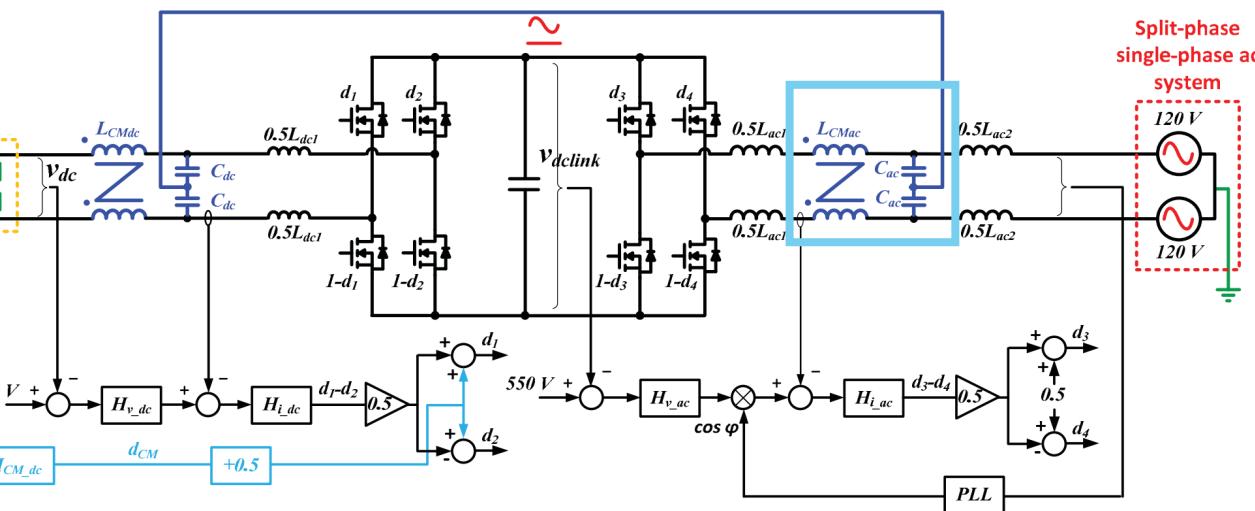**Connection** between capacitor legs are to stabilize common mode voltage



# In Conclusion:

- DC Injection mainly comes from (common mode) stray capacitance between ground and PV panels, (differential mode) ADC errors, current sensing errors and sampling circuit errors, (main injection) inverter asymmetric gate signal
- Foreign countries mainly improves control method (e.g. virtual capacitor, synchronous frame), topology (e.g. half-bridge converter, electrolytic capacitor, filter added), or sensing accuracy (e.g. demodulation)
- Back to the question: **what if inverter is malfunctioning?**
  - any control error/component malfunction will trigger OFR/UFR, OVR/OFR, HR (relays to detach PV from grid/ islanding)
  - some topology has inverter to block the DC components