

Introduction to Power System - [Lecture Hour = 2 hours]

## **Per Phase System, Three Phase Transformer & Per Unit Calculation**

Karl M.H. LAI

# Three Phase Systems

High-power equipment such as generators, transformers, and transmission lines are built as three phase equipment. However, at the distribution level, depending on the voltage/power rating, a mixture of **single phase** and **three-phase** systems is used.

The three-phase system has many advantages over the single-phase system.

1. Three-phase systems produce a rotating magnetic field inside the alternating current (ac) motors and, therefore, cause the **motors to rotate without the need for extra controls**.
2. Three-phase generators **produce more power** than single-phase generators of equivalent volume.
3. Three-phase **transmission lines transmit three times the power** of single-phase lines.
4. Three-phase systems are **more reliable**; when one phase is lost, the other two phases can still deliver some power to the loads

## Line Parameter and Phase Parameter

- Power System can be divided into three distinct parts: **source**, **transmission** and **load**.
- The currents in the transmission line conductors are called **line currents**. The voltages of the transmission line are classified by two variables: (1) **line-to-neutral voltage** and (2) **line-to-line voltage**
- The currents flowing through the source coil (generator or transformer) is **phase current**. The line-to-ground voltage is also called **phase voltage**. Phase voltage is the voltage between any line and the ground (or neutral).

# Generation of Three-Phase Voltages

- **Faraday's law:** When conductor cuts magnetic field lines, a voltage is induced across the conductor.
- The generator consists of an outer frame called **stator** and a rotating magnet (permanent magnet or DC field coil) called **rotor**.
- When the magnet is spinning clockwise inside the machine by an **external prime mover**, the magnetic field then cuts all coils and, therefore, **induces a voltage** across each of them. ( $\Phi \rightarrow V$ )
- If each coil is connected to a **load impedance**, a current would flow into the load, and the generator produces electric energy that is consumed by the load. ( $V \rightarrow I$ )
- The voltage across any of the three coils can be expressed by Faraday's law:

$$e = nBl\omega$$


$e$  is the voltage induced across the coil

$n$  is the number of turns in the coil

$B$  is the flux density of the magnetic field



$l$  is the length of the slot

$\omega$  is the angular speed

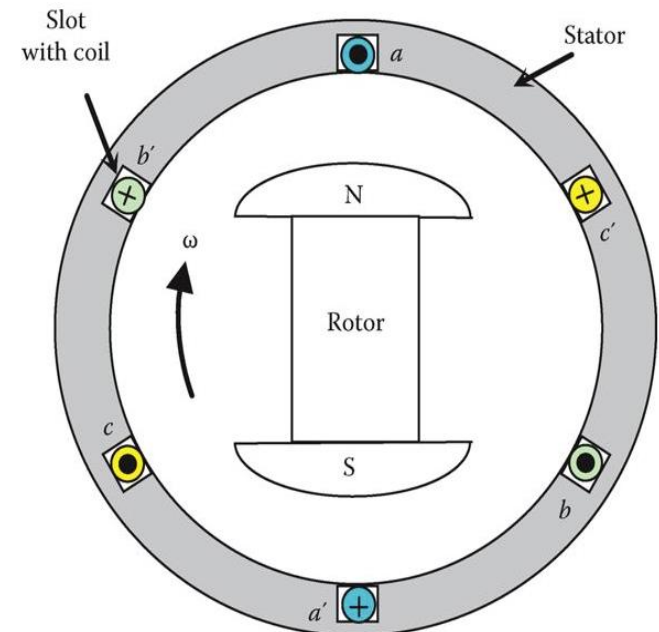

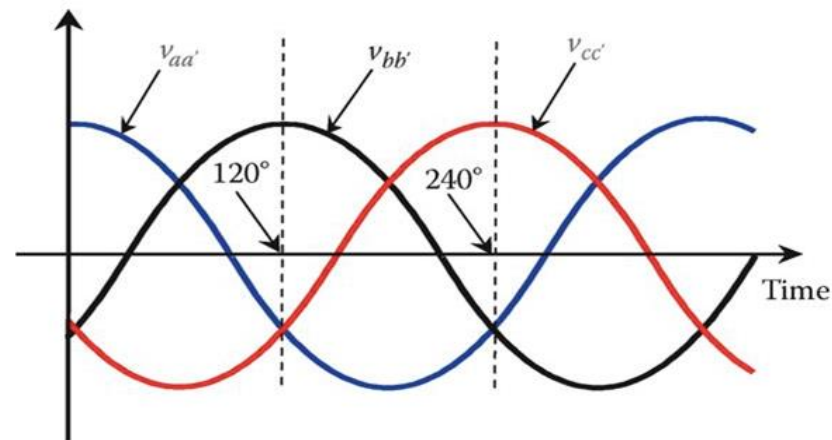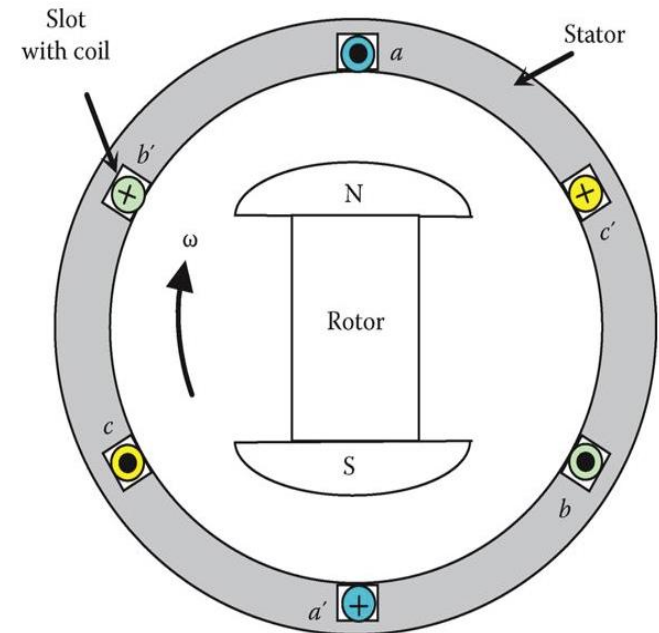
# Generation of Three-Phase Voltages

- Voltage induced is proportional to perpendicular component of the magnetic field w.r.t. conductor.
- At the rotor position in Figure, coil **a-a'** has the maximum perpendicular field and, hence, it has the maximum induced voltage. Coil **b-b'** will have its maximum voltage when the rotor moves clockwise by  $120^\circ$ , and coil **c-c'** will have its maximum voltage when the rotor is at  $240^\circ$  position.
- If the rotation is continuous, the voltage across each coil is **sinusoidal**, all coils have the same magnitude of the maximum voltage, and the induced voltages are shifted by  $120^\circ$ . → **Three Phase System**


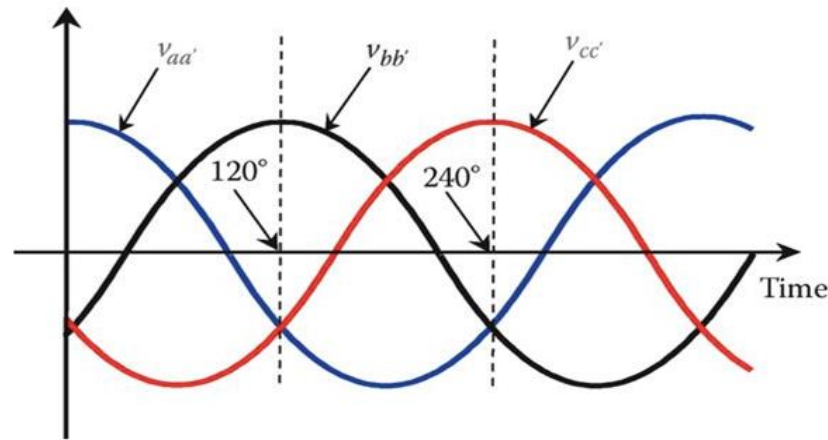
# Generation of Three-Phase Voltages: Mathematical Expression



## Time domain Representation

$$v_{aa'} = V_{max} \cos \omega t$$

$$v_{bb'} = V_{max} \cos(\omega t - 120^\circ)$$

$$v_{cc'} = V_{max} \cos(\omega t - 240^\circ)$$

where,

$\bar{V}$  is the phasor voltage in complex number form

$V$  is the magnitude of the rms voltage

## Phasor domain Representation

$$\bar{V}_{aa'} = \frac{V_{max}}{\sqrt{2}} \angle 0^\circ = V \angle 0^\circ$$




$$\bar{V}_{bb'} = \frac{V_{max}}{\sqrt{2}} \angle -120^\circ = V \angle -120^\circ$$

$$\bar{V}_{cc'} = \frac{V_{max}}{\sqrt{2}} \angle 120^\circ = V \angle 120^\circ$$
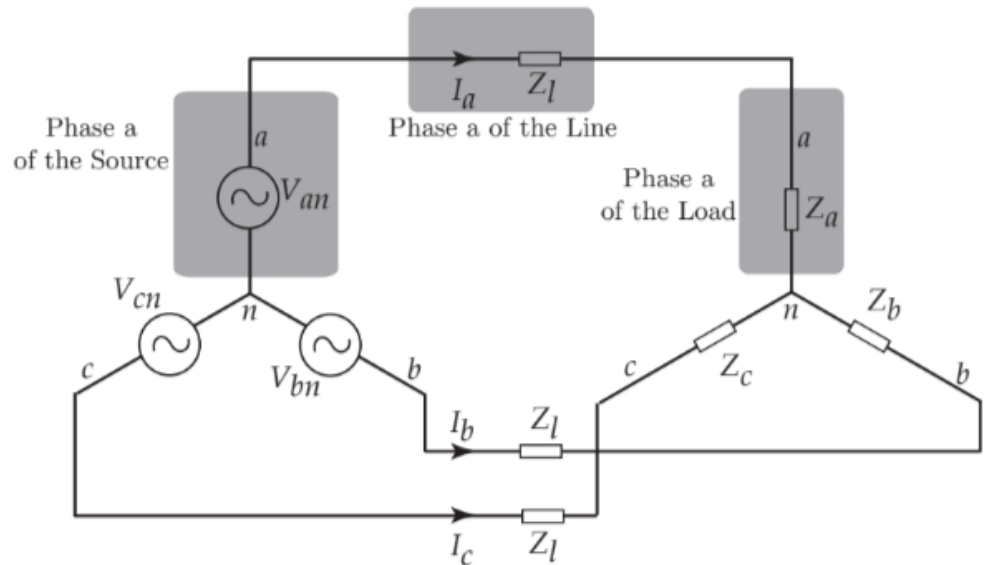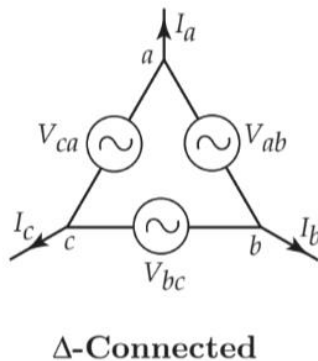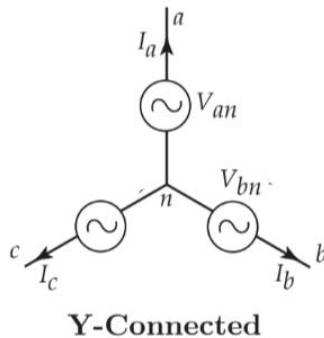
# Main Components

A **balanced 3-phase system** has:

- Three sinusoidal voltage **sources with equal magnitude**, but with a phase shift of  $120^\circ$ .
- **equal loads** on each phase.
- **equal line impedance** connecting the sources to the loads





# Y- Connected Voltage Source

$$v_{an} = V_{\max} \cos(\omega t + \alpha)$$

$$v_{bn} = V_{\max} \cos(\omega t + \alpha - 120^\circ) \longrightarrow v_{an} = V \angle \alpha$$

$$v_{cn} = V_{\max} \cos(\omega t + \alpha - 240^\circ) \longrightarrow v_{bn} = V \angle \alpha - 120^\circ$$

$$v_{cn} = V \angle \alpha - 240^\circ$$

In every balanced three-phase system, the sum of abc variables is ALWAYS zero:



$$V_{an} + V_{bn} + V_{cn} = 0$$

Line-to-Line Voltage (with  $\sqrt{3}$ ) as convention in power system.

$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} = V (1 \angle \alpha - 1 \angle (\alpha - 120^\circ)) \\ &= \sqrt{3} V \angle \alpha + 30^\circ \end{aligned}$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V \angle \alpha - 90^\circ$$
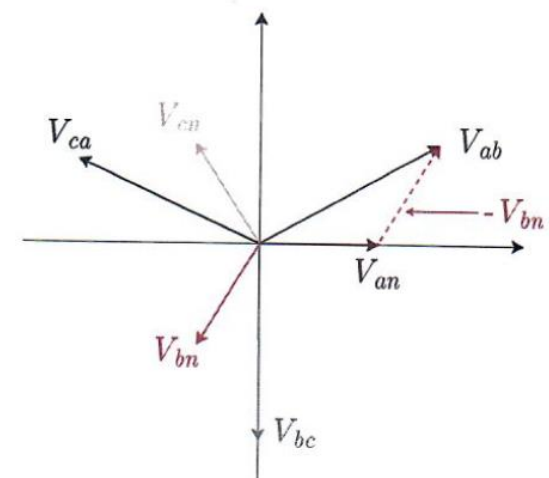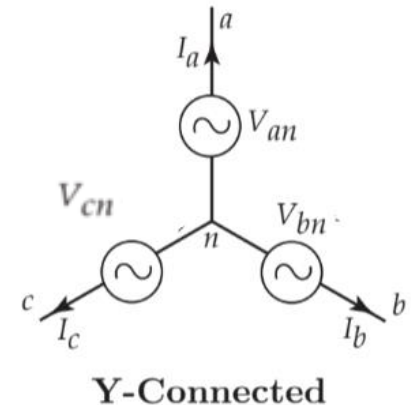
$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V \angle \alpha - 210^\circ$$



# $\Delta$ - Connected Voltage Source


For the  $\Delta$  connection, Phase voltages equal Line voltages.

For line current, it is a sum of current from the connected two sources.

$$I_a = I_{ca} - I_{ab} = \sqrt{3}I_{ca}\angle 30^\circ$$

$$I_b = I_{ab} - I_{bc} = \sqrt{3}I_{ab}\angle 30^\circ$$
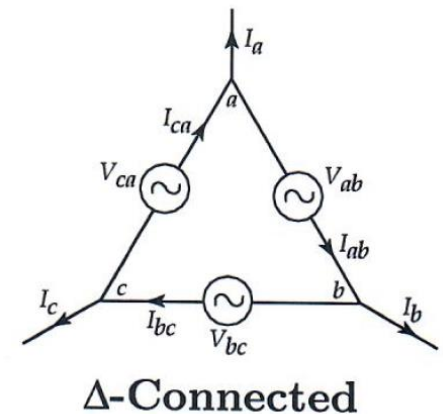
$$I_c = I_{bc} - I_{ca} = \sqrt{3}I_{bc}\angle 30^\circ$$





Line Currents are also balanced.

Measurement from outside, the currents are;  $I_a / I_b / I_c$

Measurement from outside, the voltages are;  $V_{ab} / V_{bc} / V_{ca}$

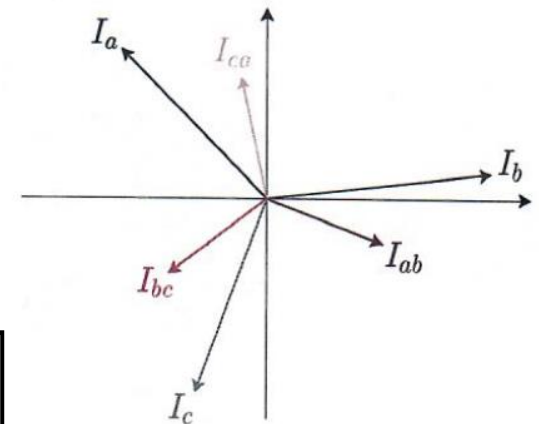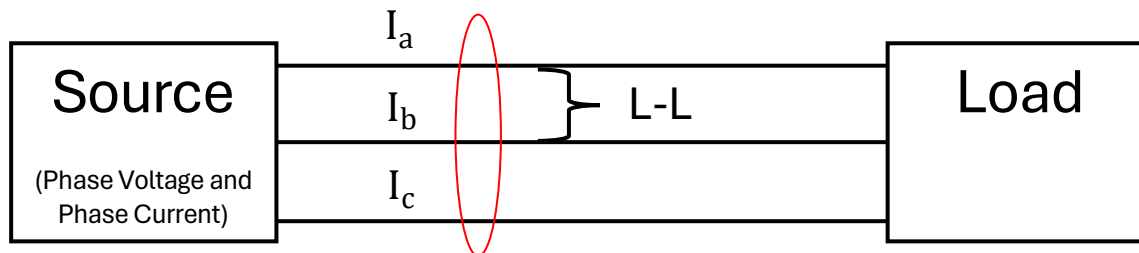**Note:** Line voltage = Phase Voltage in Delta Connection






# Y- Connected Voltage Source
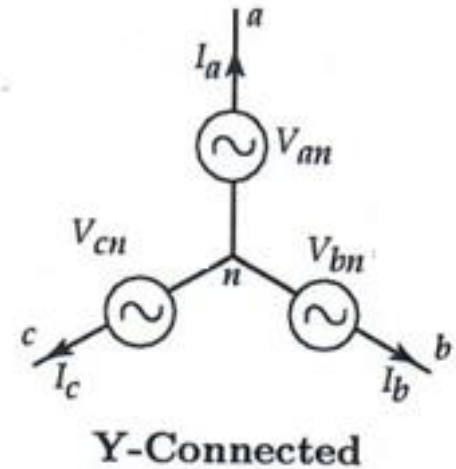
## Summary


For Y-connected source:

$$\begin{aligned}V_{\text{line}} &= \sqrt{3}V_{\text{phase}} \angle 30^\circ \\I_{\text{line}} &= I_{\text{phase}} \\S_{3-\phi} &= 3V_{\text{phase}} I^* = V_{an} \cdot I_a^* + V_{bn} \cdot I_b^* + V_{cn} \cdot I_c^*\end{aligned}$$



For  $\Delta$ -Connection source:
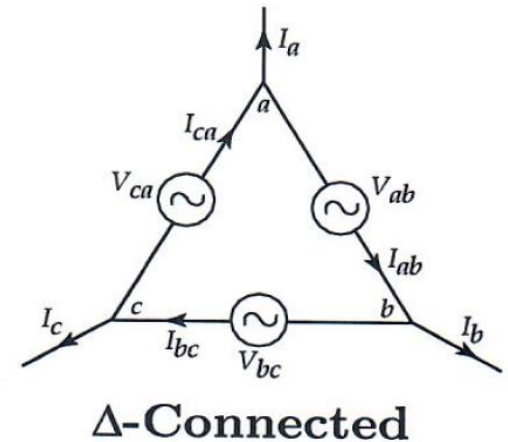
$$\begin{aligned}V_{\text{line}} &= V_{\text{phase}} \\I_{\text{line}} &= \sqrt{3}I_{\text{phase}} \angle 30^\circ \\S_{3\phi} &= 3V_{\text{phase}} I_{\text{phase}}^* = V_{ab}I_{ab}^* + V_{bc}I_{bc}^* + V_{ca}I_{ca}^*\end{aligned}$$



# Y-Connected Load and $\Delta$ -Connected Load

For **wye-connected load**:

Phase & Line Currents are the same.

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3}V_{an} \cdot e^{j30^\circ}$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3}V_{bn} \cdot e^{j30^\circ}$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3}V_{cn} \cdot e^{j30^\circ}$$



For **delta-connected load**:

Phase & Line Voltages are the same.


$$I_a = I_{ca} - I_{ab} = \sqrt{3} I_{ca} e^{j30^\circ}$$

$$I_b = I_{ab} - I_{bc} = \sqrt{3} I_{ab} e^{j30^\circ}$$
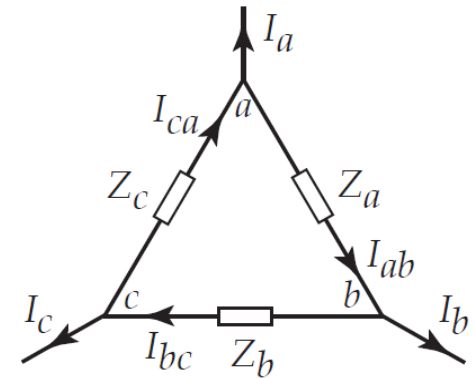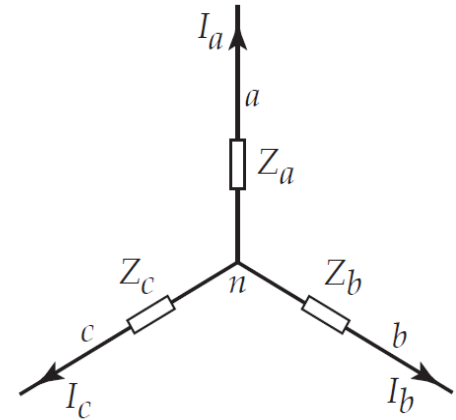
$$I_c = I_{bc} - I_{ca} = \sqrt{3} I_{bc} e^{j30^\circ}$$


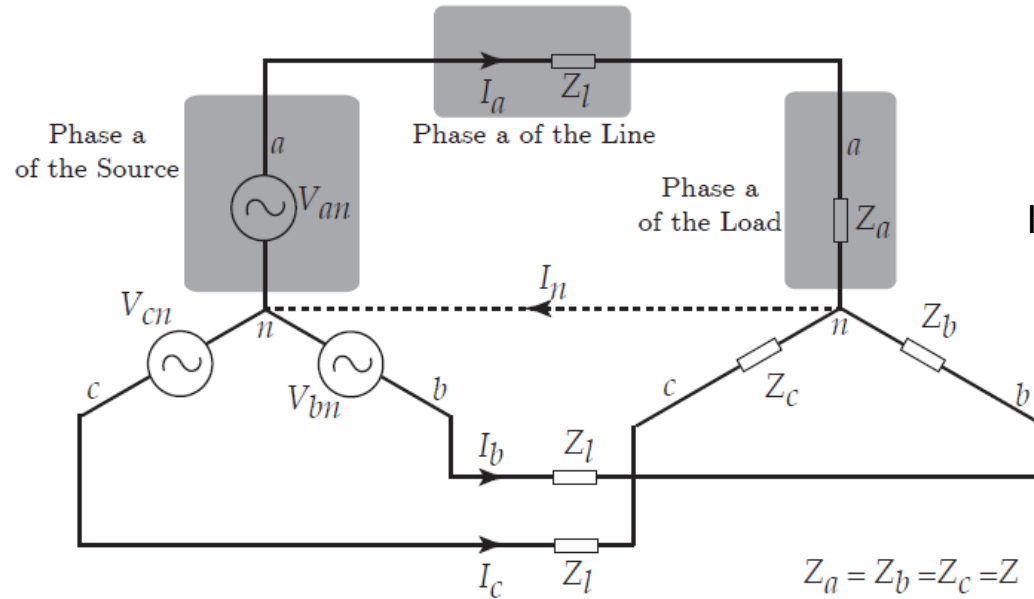
# Neutral Current and Unbalance Condition



KCL:

$$I_n = I_a + I_b + I_c$$

With KCL:  $I_n = I_a + I_b + I_c$

$$I_n = \frac{V_{an}}{Z_l + Z_a} + \frac{V_{bn}}{Z_l + Z_b} + \frac{V_{cn}}{Z_l + Z_c} = \frac{1}{Z_l + Z_a} (V_{an} + V_{bn} + V_{cn})$$

$$I_n = \frac{1}{Z_l + Z_a} (0) = 0$$

If there is any **unbalance**, in terms of source, load or lines, there is **neutral voltage shift** and **neutral current flow**. It is important in sizing neutral conductor and design earthing system.

## Example 1 - Delta Load with Wye Source

Assume a  $\Delta$ -connected load is supplied from a 3-phase 13.8kV (L-L) source with  $Z = 100\angle 20^\circ \Omega$ .

(a) Find  $I_a$ ,  $I_b$ , and  $I_c$ .

(b) Determine the load apparent power of the source.

### Solution

$$V_{ab} = 13.8\angle 0^\circ \text{ kV}$$


$$V_{bc} = 13.8\angle -120^\circ \text{ kV}$$

$$V_{ca} = 13.8\angle -240^\circ \text{ kV}$$

$$I_{ab} = \frac{13.8\text{ k}\angle 0^\circ}{100\angle 20^\circ} = 138\angle -20^\circ \text{ A}$$

$$I_{bc} = \frac{13.8\text{ k}\angle -120^\circ}{100\angle 20^\circ} = 138\angle -140^\circ \text{ A}$$
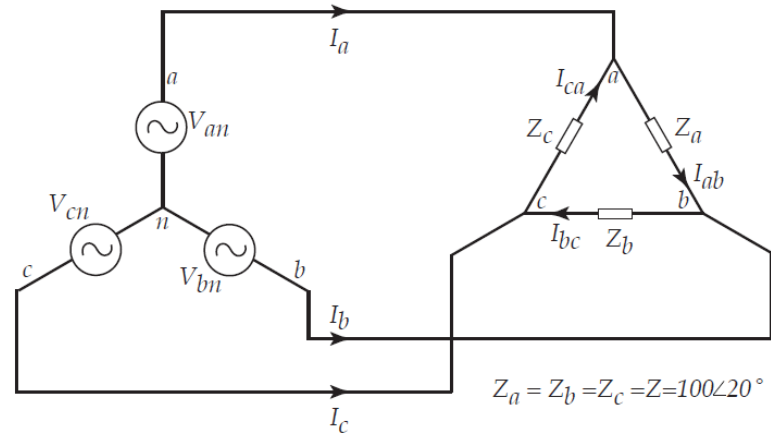
$$I_{ca} = \frac{13.8\text{ k}\angle -240^\circ}{100\angle 20^\circ} = 138\angle -260^\circ \text{ A}$$



## Example 1 (Delta Load with Wye Source) cont'

From phase component to line component:


$$I_a = I_{ab} - I_{ca} = (138\angle -20^\circ) - (138\angle -260^\circ)$$

$$I_a = 239\angle -50^\circ \text{ A}$$

$$I_b = 239\angle -170^\circ \text{ A}$$

$$I_c = 239\angle -290^\circ \text{ A}$$
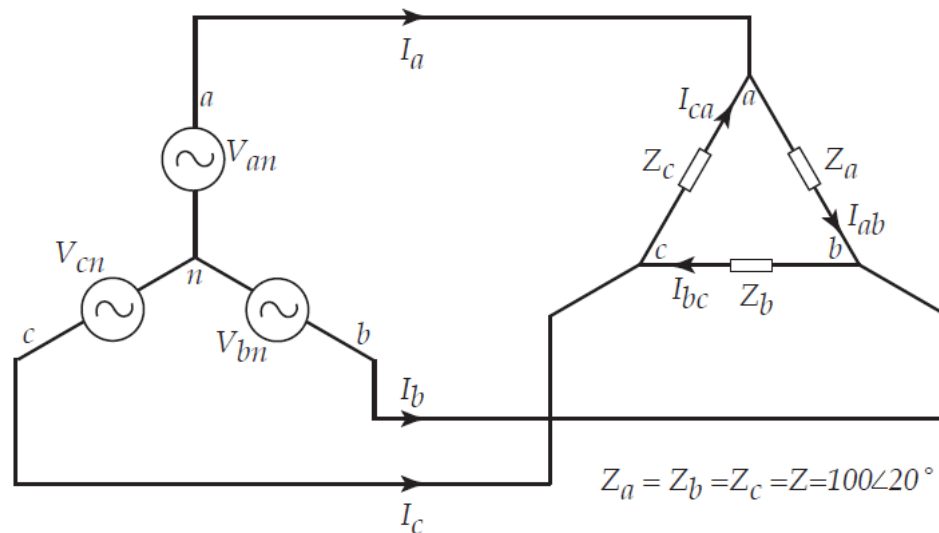
$$S = 3 \times V_{ab} I_{ab}^* = 3 \times 13.8\angle 0^\circ \text{ kV} \times 138\angle 20^\circ = 5.7\angle 20^\circ \text{ MVA} = 5.37 + j1.95 \text{ MVA}$$



# $\Delta$ - Y Transformation

To simplify analysis of balanced 3 Phase systems:

- $\Delta$ -connected sources can be replaced by an equivalent Y-connected sources with

$$V_{\text{phase},Y} = \frac{V_{\text{line},\Delta}}{\sqrt{3} \angle 30^\circ}$$

- $\Delta$ -connected loads can be replaced by an equivalent Y-connected loads with




$$Z_Y = \frac{Z_\Delta}{3}$$

For the source,

$$V_{ab,Y} = V_{an,Y} - V_{bn,Y} = \sqrt{3}V_{an,Y} \angle 30^\circ$$

$$V_{ab,\Delta} = \sqrt{3}V_{an,Y} \angle 30^\circ$$
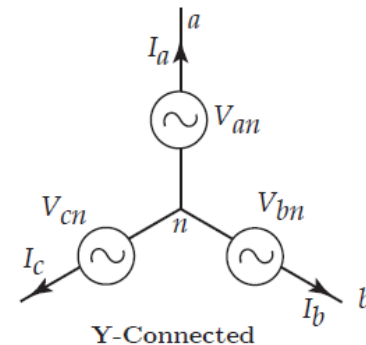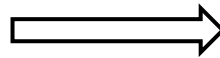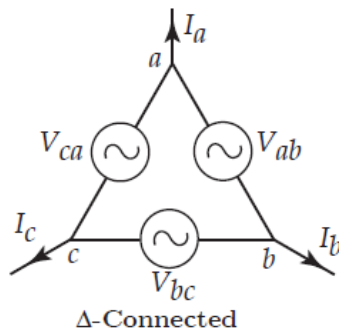
$$V_{an,Y} = \frac{V_{ab,\Delta}}{\sqrt{3}} \angle -30^\circ$$





# Three Phase Transformers Combinations

Three phase transformers are of  $\Delta - \Delta$ , Y - Y,  $\Delta - Y$ , and Y -  $\Delta$  combinations.

## $\Delta - \Delta$

- Common in Transmission Systems
- Reliability
- 3rd harmonics propagation
- Cannot be grounded
- Cannot supply very unbalanced system
- cannot handle a large amount of single-phase load.


## Y - Y

- Can be grounded on each side.
- No phase shift
- No 3rd harmonics propagation.

## $\Delta - Y$


- Most commonly used connection scheme (Step-down transformer between Transmission and Distribution).
- Presence of Neutral/ Can be grounded.
- 3rd harmonics propagation.
- Reliable
- Phase shift

# Δ- Y Transformation - Loads

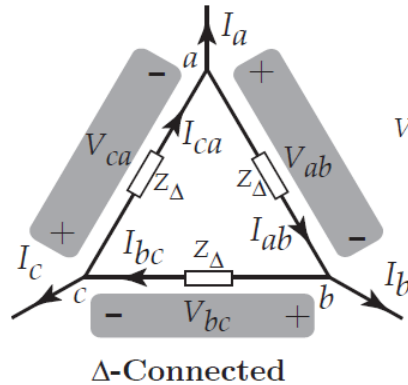

Equivalent if:
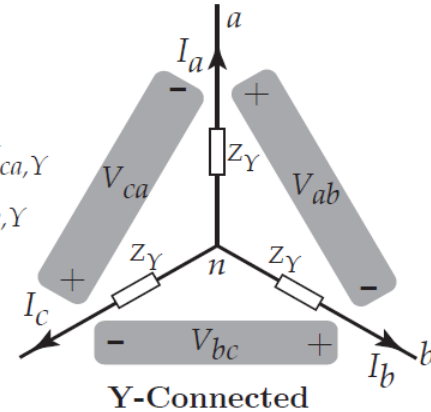
$$\begin{array}{lll} V_{ab,\Delta} = V_{ab,Y} & V_{bc,\Delta} = V_{bc,Y} & V_{ca,\Delta} = V_{ca,Y} \\ I_{a,\Delta} = I_{a,Y} & I_{b,\Delta} = I_{b,Y} & I_{c,\Delta} = I_{c,Y} \end{array}$$



From Δ-side: we have,

$$I_a = I_{ca} - I_{ab} = \frac{V_{ca}}{Z_{\Delta}} - \frac{V_{ab}}{Z_{\Delta}} = \frac{V_{ca} - V_{ab}}{Z_{\Delta}}$$

From Y-side: we have,

$$V_{ab} = V_{an} - V_{bn} = I_b \cdot Z_Y - I_a \cdot Z_Y \quad V_{ca} = V_{cn} - V_{an} = I_a \cdot Z_Y - I_c \cdot Z_Y$$

$$V_{ca} - V_{ab} = Z_Y(2I_a - I_b - I_c)$$

$$I_a + I_b + I_c = 0 \Rightarrow I_a = -I_b - I_c \cdot \frac{Z_0}{3}$$

$$Z_Y = \frac{Z_{\Delta}}{3}$$

$$V_{ca} - V_{ab} = Z_Y \cdot 3I_a$$

# Per Phase Analysis

Per phase analysis allows analysis of balanced 3-phase systems with the same effort as for a single-phase system. Per phase analysis is applicable to balanced 3-phase systems with all loads and sources Y-connected and no mutual inductance between phases.

In such systems:

- All neutrals are at the same potential.
- All phases are COMPLETELY *decoupled*.
- All system values are the same sequence as sources. The sequence order we have been using (phase b lags phase a and phase c lags phase b ) is known as positive sequence.
- Convert all  $\Delta$  load/sources to equivalent Y's.
- Keep in mind that all neutrals are at the same potential.


Procedures -

1. Solve phase "a" independent of the other phases.
2. Total system power is then  $S = 3V_a I_a^*$ .
3. If desired, phase "b" and "c" values can be determined by inspection (i.e.,  $\pm 120^\circ$  degree phase shifts).
4. If necessary, go back to original circuit to determine line-line values or internal  $\Delta$  values.

## Example 2 - Per Phase Analysis

Assume a 3 phase, Y-connected generator with  $V_{an} = 1\angle 0^\circ$  volts supplies a  $\Delta$ -connected load with  $Z_\Delta = -j$  through a transmission line with impedance of  $0.1j$  per phase. The load is also connected to a  $\Delta$  connected generator with  $V_{ab} = 1\angle 0^\circ$  through a second transmission line which also has an impedance of  $j0.1$  per phase. Find:

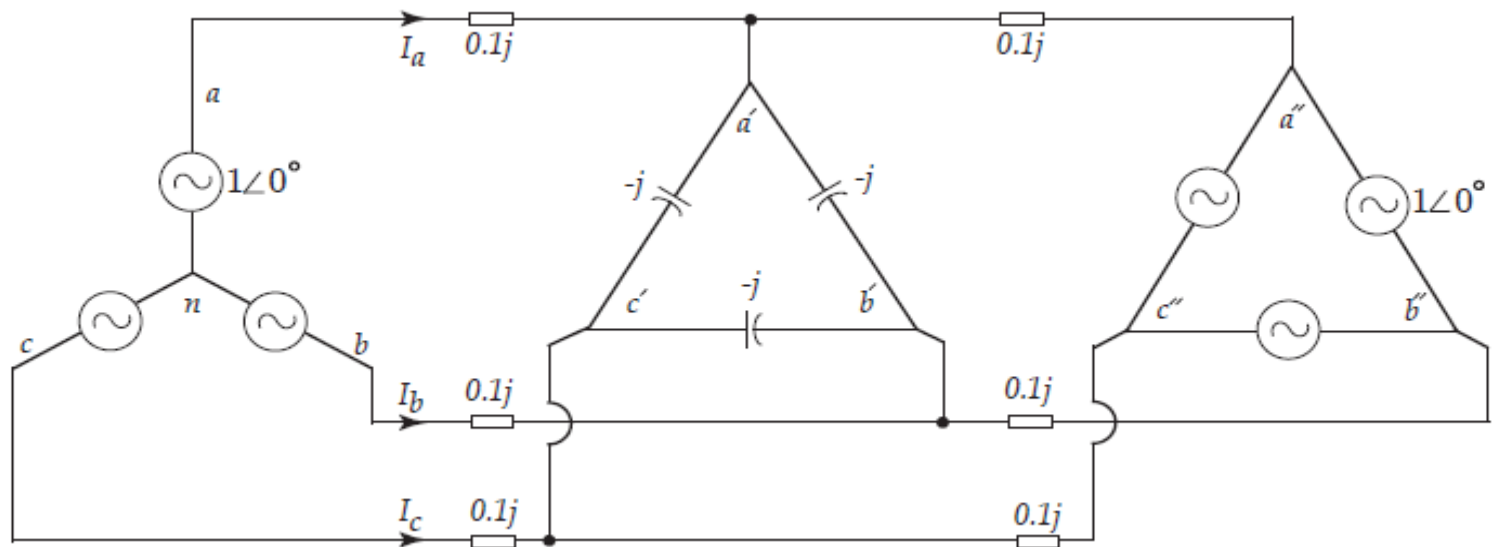
- (a) load voltage  $V_{a'b'}$
- (b) The total power supplied by each generator,  $S_Y$  and  $S_\Delta$ .




## Example 2 - Per Phase Analysis

### Solution

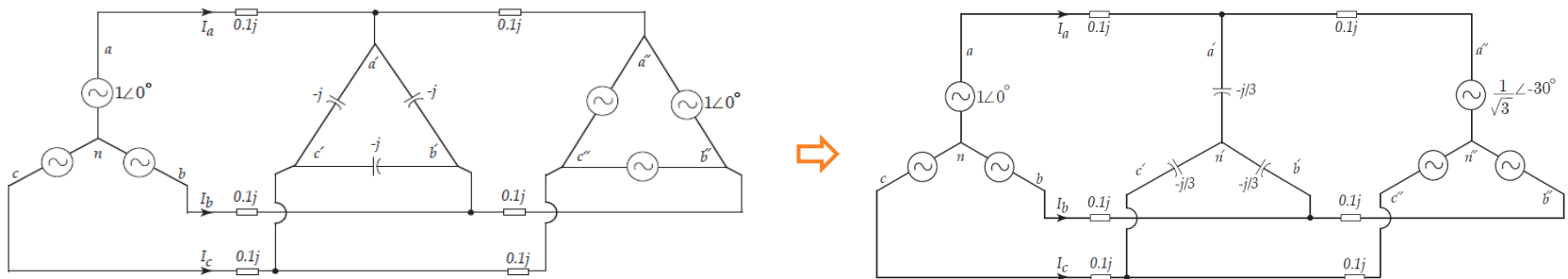1. Convert all delta source and load into wye.



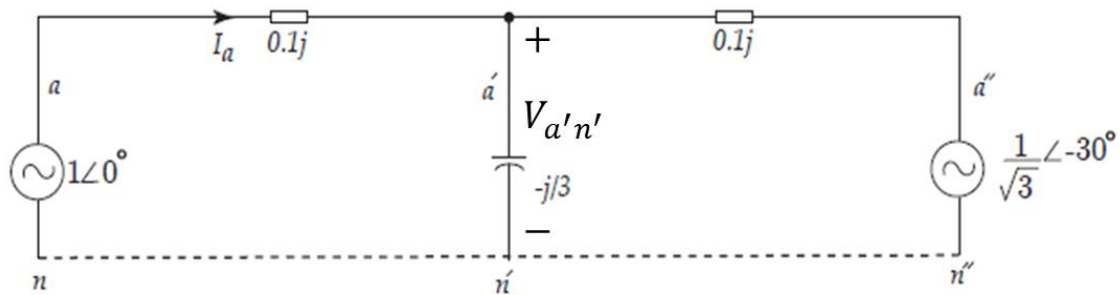2. Since it is a balanced network, put it in per phase analysis.



KCL at a': 
$$(V_{a'n'} - 1\angle 0^\circ)(-10j) + V_{a'n'}(3j) + \left(V_{a'n'} - \frac{1}{\sqrt{3}}\angle -30^\circ\right)(-10j) = 0$$

## Example 2 - Per Phase Analysis

Therefore,

$$\left(10j + \frac{10}{\sqrt{3}} \angle 60^\circ\right) = V_{a'n'}(10j - 3j + 10j) \rightarrow V_{a'n'} = 0.9 \angle -10.9^\circ \text{ V}$$

3. Obtain other two phase voltages with from the reference phase by shifting  $120^\circ$ .

$$V_{a'n'} = 0.9 \angle -10.9^\circ \text{ V}$$

$$V_{b'n'} = 0.9 \angle -130.9^\circ \text{ V} \quad V_{c'n'} = 0.9 \angle -250.9^\circ \text{ V}$$

4. Put it in phase voltage with the conversion factor.

$$V_{a'b'} = V_{a'n'} - V_{b'n'} = 1.56 \angle 19.1^\circ \text{ V}$$

5. Calculate the source power [VA] and load power [VA]

$$S_{Y, \text{Gen}} = 3V_{an}I_a^* = 3V_{an} \left( \frac{V_{an} - V_{a'n'}}{j0.1} \right)^* = 5.1 + j3.5 \text{ VA}$$

$$S_{\Delta, \text{Gen}} = 3V_{a''n''}I_{a''}^* = 3V_{a''n''} \left( \frac{V_{a''n''} - V_{a'n'}}{j0.1} \right)^* = -5.1 - j4.7 \text{ VA}$$

Note: We calculate the complex power in the transformed circuit. Since  $\Delta$  source and its transformed Y source are equivalent, their complex power is the same.




## Example 3 - Per Phase Analysis

Assume a 3-phase,  $\Delta$ -connected generator with  $V_{ab} = 2\angle 0^\circ$  volts supplies a  $\Delta$ -connected load with  $Z_\Delta = -3j\Omega$  through a transmission line with impedance of  $0.1j\Omega$  per phase. The load is also connected to another Y-connected load with impedance of  $Z_{\text{load}}$  through a second transmission line which has an impedance of  $0.2j\Omega$  per phase.

Calculate the complex power of the second load for two scenarios:

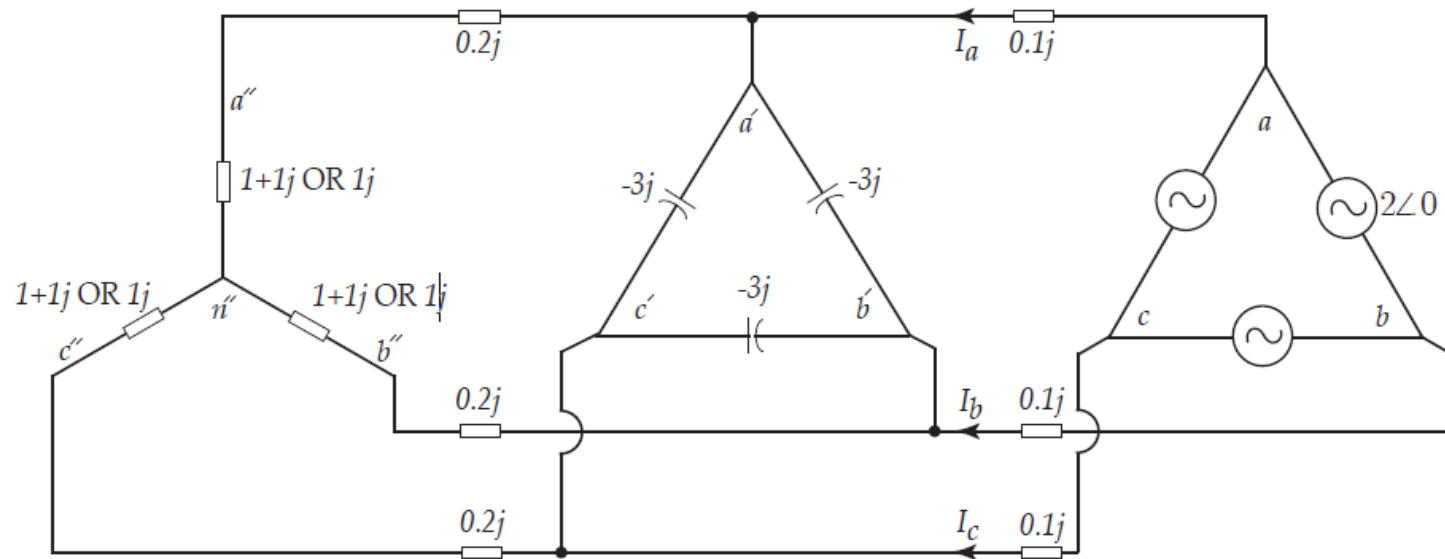
- i)  $Z_{\text{load}} = j1\Omega$  and ii)  $Z_{\text{load}} = 1 + j1\Omega$




## Example 3 - Per Phase Analysis

### Solution

1. Convert all delta into wye.

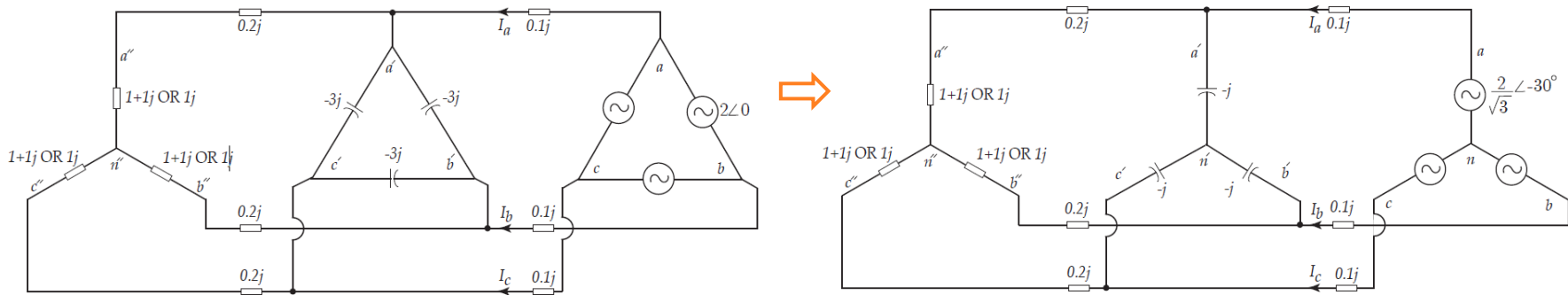

2. Put it in per phase analysis.

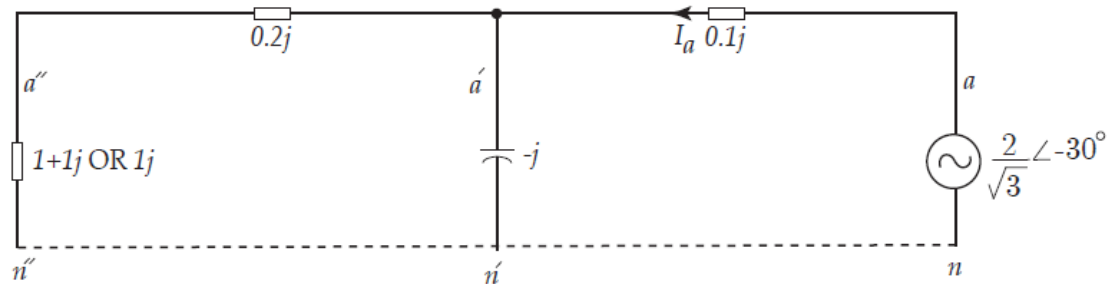

By KCL:

$$\frac{V_{a'n'}}{0.2j + 1 + 1j} + \frac{V_{a'n'}}{-j} + \frac{V_{a'n'} - \frac{2}{\sqrt{3}} \angle -30^\circ}{0.1j} = 0$$

## Example 3 - Per Phase Analysis

Therefore, 
$$\frac{-20}{\sqrt{3}} \angle 60^\circ = V_{a'n'} \left( \frac{1}{1 + 1.2j} + j - 10j \right) \rightarrow V_{a'n'} = 1.21 \angle -32.47^\circ \text{ V}$$

$$I_{load\ 1,a} = \frac{V_{a'n'}}{1 + 1j + 0.2j} = 0.78 \angle -82.66^\circ \text{ A}$$

$$V_{a''n''} = I_{load\ 1,a} (1 + 1j) = 1.1 \angle -37.68^\circ \text{ V}$$

$$S_{load\ 1} = 3V_{a''n''} I_{load\ 1,a}^* = 1.81 + j1.81 \text{ VA}$$

For another load:  $1 + j1\Omega$ , with KCL: 
$$\frac{V_{a'n'}}{0.2j + 1j} + \frac{V_{a'n'}}{-j} + \frac{V_{a'n'} - \frac{2}{\sqrt{3}} \angle -30^\circ}{0.1j} = 0$$

$$\frac{-20}{\sqrt{3}} \angle 60^\circ = V_{a'n'} \left( \frac{1}{1.2j} + j - 10j \right) \rightarrow V_{a'n'} = 1.17 \angle -30^\circ \text{ V}$$

$$I_{load\ 2,a} = \frac{V_{a'n'}}{1j + 0.2j} = 0.98 \angle -120^\circ \text{ A}$$

$$V_{a''n''} = I_{load\ 2,a} (1j) = 0.98 \angle -30^\circ \text{ V}$$

$$S_{load\ 2} = 3V_{a''n''} I_{load\ 2,a}^* = 0 + j2.87 \text{ VA}$$

# Key Messages

- Three-phase systems are usually used at high power/voltage levels.
- Three-phase systems are more economical for transferring energy as they need less amount of wire to transmit the same amount of energy compared to single or two-phase systems.
- To analyze complicated three-phase BALANCED systems,  $\Delta - Y$  transformation is the key element.
- In three-phase BALANCED systems, when all  $\Delta$  loads and sources are transformed to  $Y$  connections, neutral points are at the same potential. Hence, per phase analysis can be applied.

# Power in Single Phase Circuits

- The instantaneous power delivered to a load is,

$$\begin{aligned} p(t) &= v(t)i(t) \\ &= \sqrt{2} V \sin \omega t \sqrt{2} I \sin(\omega t - \phi) \\ &= VI \cos \phi - VI \cos(2\omega t - \phi) \end{aligned}$$

- This power clearly has an average value,  $P = VI \cos \phi$  (W). This is referred to as the "real power." The second, double frequency, term has no time averaged value, and therefore does no work.
- $\cos \phi$  is the "power factor"
- "Reactive Power,"  $Q = VI \sin \phi$  (VAR)
- $Q > 0 \Rightarrow \phi > 0 \Rightarrow R - L$  load (motor, wires).  $Q < 0 \Rightarrow \phi < 0 \Rightarrow R - C$  load (battery).
- Complex Power,  $S = P + jQ = VI^*$  ( \* is complex conjugate )

# Power in Three Phase Circuits

- The instantaneous power is:

$$p(t) = p_a(t) + p_b(t) + p_c(t)$$

$$p_a(t) = \sqrt{2}V_{an}\cos(\omega t)\sqrt{2}I_a\cos(\omega t - \phi)$$

$$p_b(t) = \sqrt{2}V_{an}\cos(\omega t - 2\pi/3)\sqrt{2}I_a\cos(\omega t - 2\pi/3 - \phi)$$

$$p_c(t) = \sqrt{2}V_{an}\cos(\omega t + 2\pi/3)\sqrt{2}I_a\cos(\omega t + 2\pi/3 - \phi)$$

$$\begin{aligned} p(t) &= 2V_{an}I_a \left[ \cos(\omega t) \sqrt{2} \cos(\omega t - \phi) + \cos\left(\omega t - \frac{2\pi}{3}\right) \cos\left(\omega t - \frac{2\pi}{3} - \phi\right) + \cos\left(\omega t + \frac{2\pi}{3}\right) \cos(\omega t) \right] \\ &= V_{an}I_a \left[ \cos(2\omega t - \phi) \cos(\phi) + \cos\left(2\omega t - \frac{4\pi}{3} - \phi\right) \cos(\phi) + \cos\left(2\omega t + \frac{4\pi}{3} - \phi\right) \cos(\phi) \right] \\ &= 3V_{an}I_a \cos(\phi) = P \end{aligned}$$

3 x power with one more wire compared to single phase



# Ideal Transformers

First, we review the voltage/current relationships for an **ideal transformer** assuming

- no real power losses,
- magnetic core has infinite permeability,
- no leakage flux.

Primary is usually the side with the higher voltage, but may be the low voltage side on a generator step-up transformer.

Assume we have flux  $\phi_m$  in magnetic material. Then:

$$\lambda_1 = N_1 \phi_m \text{ and } \lambda_2 = N_2 \phi_m$$

$$v_1 = \frac{d\lambda_1}{dt} = N_1 \frac{d\phi_m}{dt} \text{ and } v_2 = \frac{d\lambda_2}{dt} = N_2 \frac{d\phi_m}{dt}$$


$$\frac{d\phi_m}{dt} = \frac{v_1}{N_1} = \frac{v_2}{N_2} \rightarrow \frac{v_1}{v_2} = \frac{N_1}{N_2} = a = \text{turn ratio}$$

Faraday's Law:

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

Flux Balance:

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

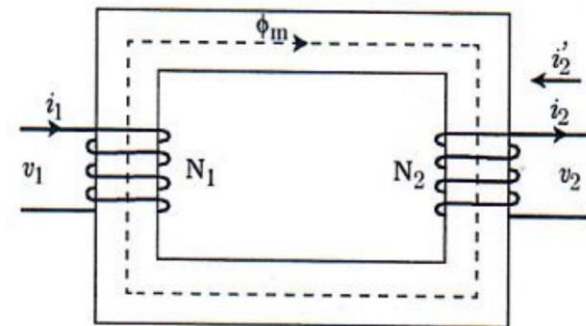

# Current/Voltage Relationships

To get the current relationships, use ampere's law:

$$\oint H \cdot dl = N_1 i_1 + N_2 i'_2 = N_1 i_1 - N_2 i_2$$

where,  $i'_2 = -i_2$


$$\frac{BL}{\mu} = HL = N_1 i_1 + N_2 i'_2$$

Assuming uniform flux density in the core,

$$\frac{\phi_m \times \text{length}}{\mu \times \text{area}} = N_1 i_1 + N_2 i'_2$$

If  $\mu$  is infinite, then  $0 = N_1 i_1 + N_2 i'_2$
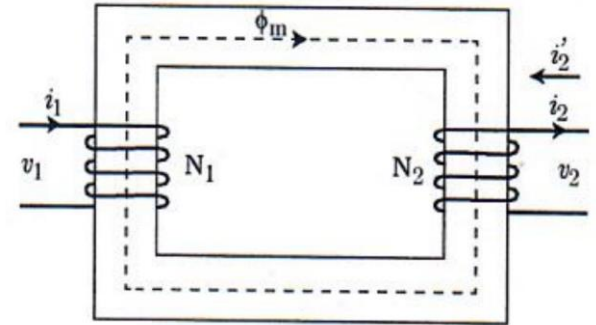
$$\frac{i_1}{i_2} = \frac{N_2}{N_1} = \frac{1}{a}$$



Matrix Form:

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} a & 0 \\ 0 & \frac{1}{a} \end{bmatrix} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

## Polarity

- Current owing into a dot on the primary winding will induce a current owing out of the dot on the corresponding secondary winding.
- Depending on how the windings are connected to the bushings, the polarities can be additive or subtractive.

# Impedance Transformation

Calculate the primary voltage and current for an impedance load on the secondary.

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} a & 0 \\ 0 & \frac{1}{a} \end{bmatrix} \begin{bmatrix} v_2 \\ \frac{v_2}{Z} \end{bmatrix}$$

$$v_1 = av_2 \text{ and } i_1 = \frac{v_2}{aZ}$$

$$Z_{eq} = \frac{v_1}{i_1} = \frac{av_2}{\frac{v_2}{aZ}} = a^2Z$$

$$Z_1 = a^2Z_2$$


This is the equivalent impedance in primary side.

Reflecting the impedance from LV side to HV side, the impedance is amplified.

# Real Transformer and Transformer Losses
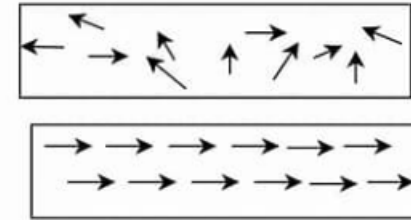
## Real Transformers

- have losses,
- have leakage flux,
- have finite permeability of magnetic core.




## Transformer Losses

Real power losses are due to **winding losses** ( $i^2 R$ ) and **core losses** due to eddy currents and hysteresis.

**Eddy currents** arise because of **changing flux** in core. Eddy currents are reduced by laminating the core.

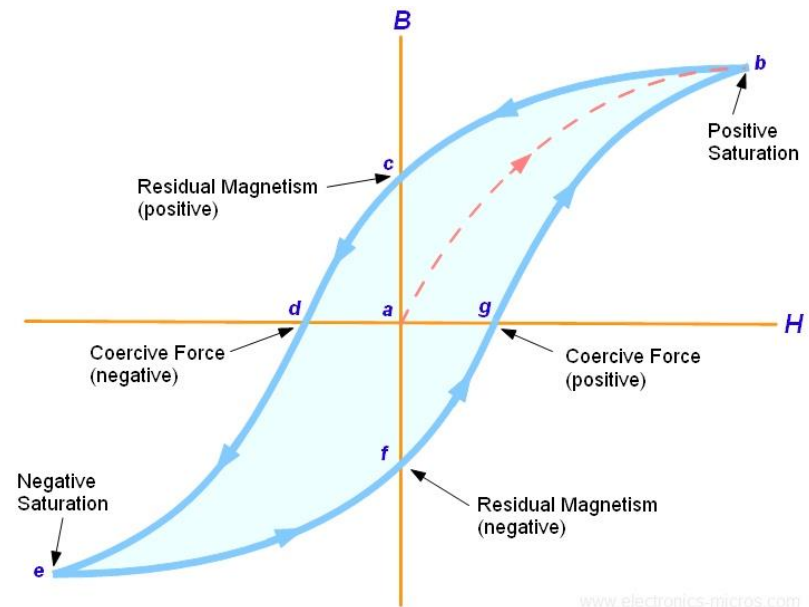**Hysteresis losses** are proportional to area of BH curve and the frequency. These losses are reduced by using material with a thin BH curve.



# Effect of Leakage Flux

Not all flux is within the transformer core.

$$\lambda_1 = \lambda_{l1} + N_1 \phi_m$$

$$\lambda_2 = \lambda_{l2} + N_2 \phi_m$$

Assuming a linear magnetic medium, we get:

$$\lambda_{l1} \triangleq L_{l1} i_1 \text{ and } \lambda_{l2} \triangleq L_{l2} i_2'$$

Thus,


$$v_1 = r_1 i_1 + L_{l1} \frac{di_1}{dt} + N_1 \frac{d\phi_m}{dt}$$

$$v_2 = r_2 i_2' + L_{l2} \frac{di_2'}{dt} + N_2 \frac{d\phi_m}{dt}$$

Winding  
Resistance

Voltage induced  
by flux leakage

Voltage  
induced by  $\phi_m$

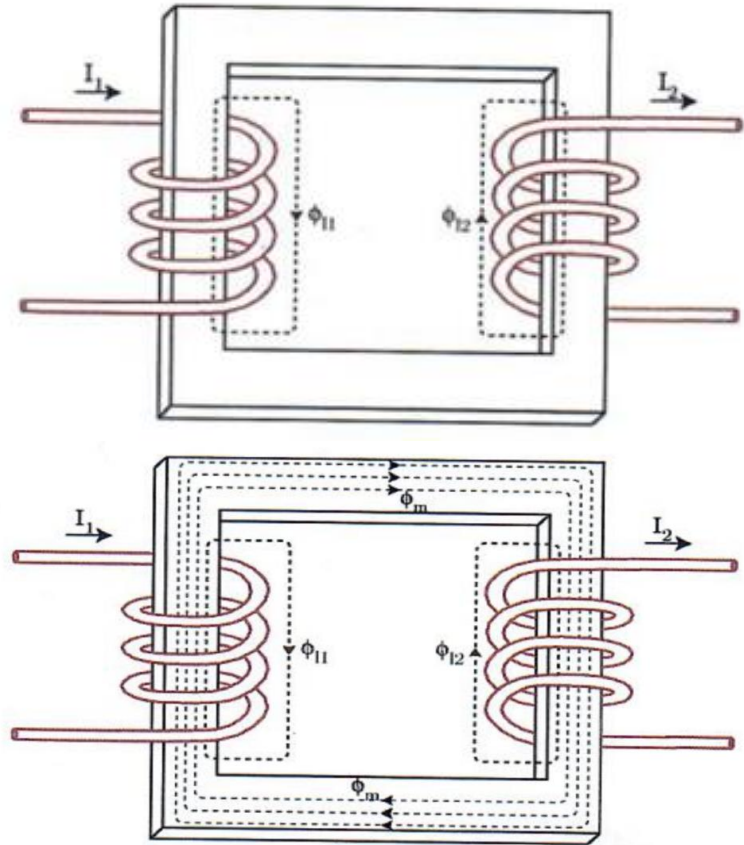

# Effect of Finite Core Permeability


Finite core permeability means a non-zero mmf is required to maintain  $\phi_m$  in the core:

$$N_1 i_1 - N_2 i_2 = \frac{\text{length}}{\mu \times \text{area}} \phi_m = \boxed{\mathcal{R} \phi_m}$$

This value is usually modelled as **magnetizing current**.

$$i_1 = \frac{\mathcal{R} \phi_m}{N_1} + \frac{N_2}{N_1} i_2 = i_m + \frac{N_2}{N_1} i_2$$


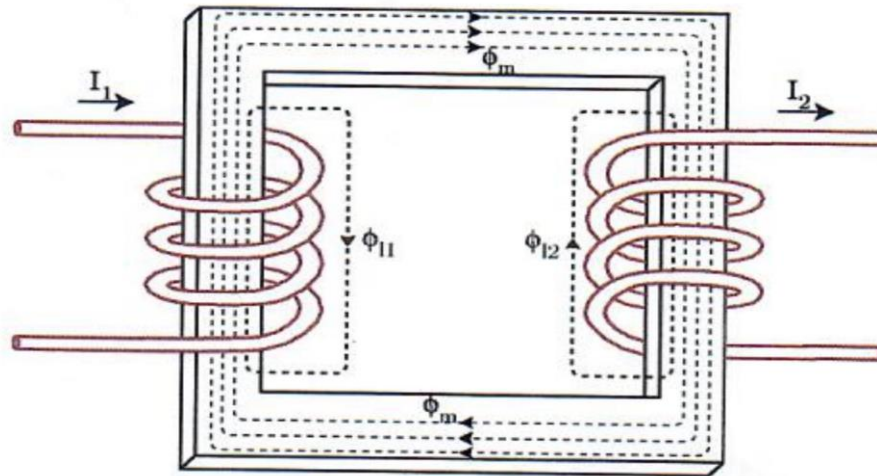
where  $i_m = \mathcal{R} \phi_m / N_1$  is the magnetizing current.




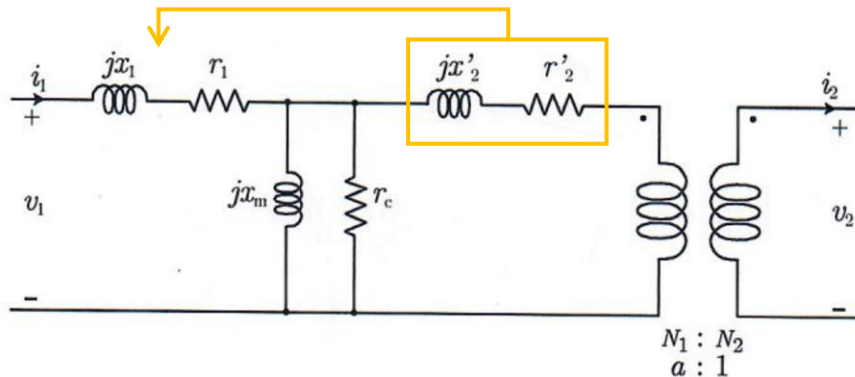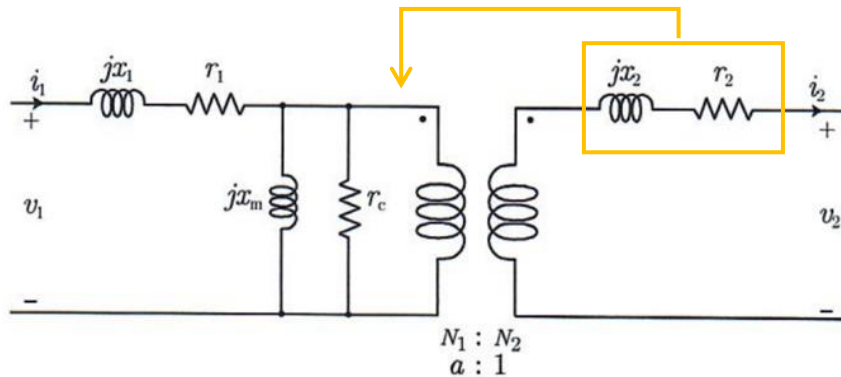
# Transformer Equivalent Circuit

- Using the previous relationships, we can derive an equivalent circuit model for the real transformer.




This model is further simplified by referring all impedances to the primary side:

$$r'_2 = a^2 r_2 \quad x'_2 = a^2 x_2$$

Moreover, since the impedance of the parallel branch is so high, approximate the equivalent circuit:
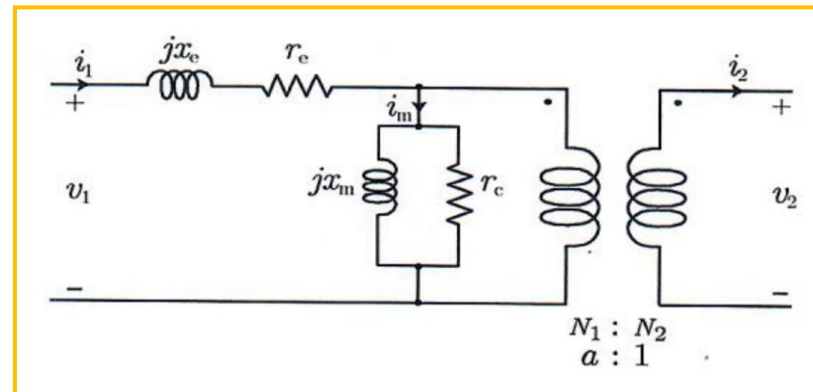
$$r_e = r_1 + r'_2 \quad x_e = x_1 + x'_2$$



# Calculation of Model Parameters

The parameters of the model are determined based upon:

- **Nameplate data:** Given rated voltages and power.
- **Open circuit test:** Rated voltage is applied to primary with secondary open; measure the primary current and losses (the test may also be done applying the voltage to the secondary, calculating the values, then referring the values back to the primary side).
- **Short circuit test:** With secondary shorted, apply voltage to primary to get rated current to flow; measure voltage and losses.

MFG	WESTINGHOUSE	SN.	PLR 4675	Hz.	60
KVA	7500/9375/10500	RISE C	55/65	% IMP	6.67
HV	138000	BIL KV	550	CLASS	QA / FA
LV	13800Y / 7967	BIL KV	110	DT. NO.	109-707


APPROX. WT. LBS.	
UNTANK WT.	22500
TANK & FIT. WT.	18700
LIQUID WT.	23800
TOTAL WT.	65000
3175 GALS.	OIL

HIGH VOLTAGE	AMPS 10500 KVA	TAP CHANGER
144900	41.8	1
141450	42.9	2
138000	43.9	3
134550	45.1	4
131100	46.2	5


LOW VOLTAGE	AMPS 10500 KVA
13800	459


# Open Circuit Test

- **Open circuit test** is conducted to determine the parameters of the magnetizing branch:  $x_m, r_c$ .
- In this test, **HV side is open-circuited**, and rated voltage is applied to LV side.
- Current, voltage, and power at LV side are measured.
- In such a case, the voltage drop in the leakage inductance and winding resistance is negligible due to very low primary current. Therefore, the transformer equivalent circuit is as shown below.

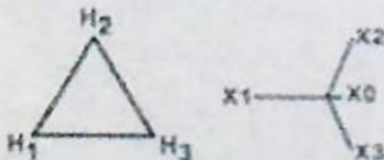
Measurement Circuit:

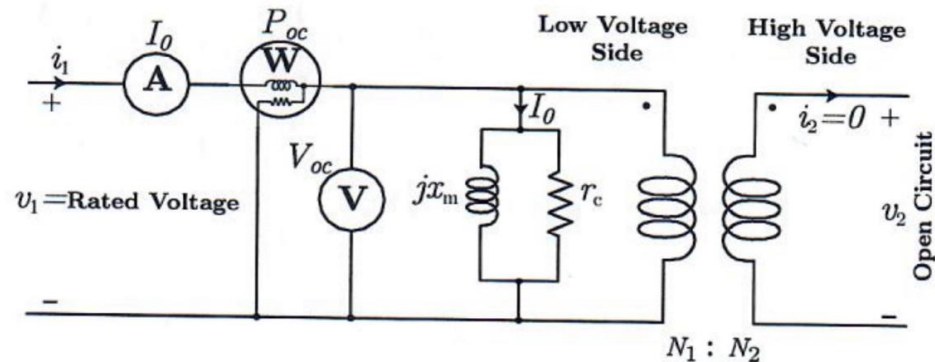

Simplified Equivalent Circuit:

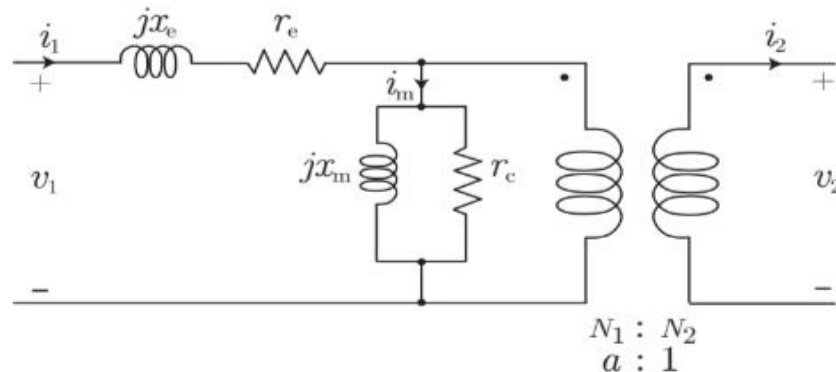

# Open Circuit Test

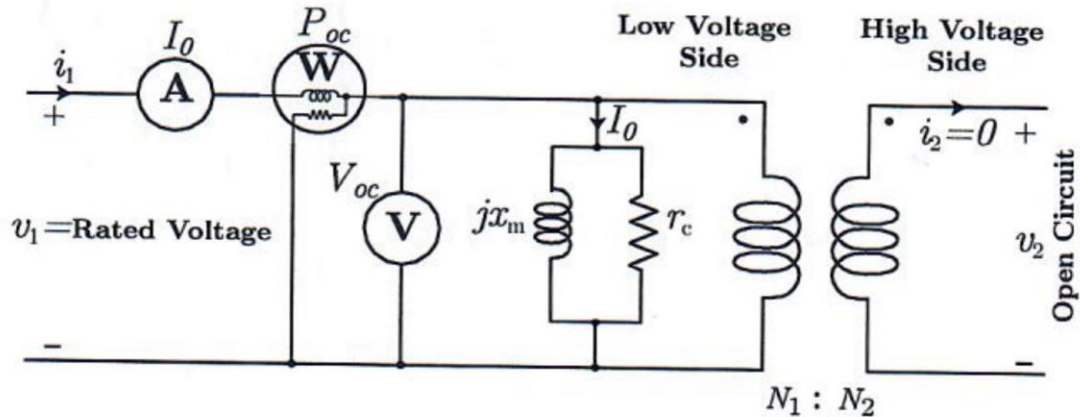

The watt-meter shows the core loss. Therefore,

$$r_c = \frac{V_{oc}^2}{P_{oc}}$$

Moreover, the magnitude of the admittance of the branch is:

$$\left\| \frac{1}{r_c} + \frac{1}{jx_m} \right\| = \sqrt{\frac{1}{r_c^2} + \frac{1}{x_m^2}} = \frac{I_0}{V_{oc}} \rightarrow x_m = \frac{1}{\sqrt{\left(\frac{I_0}{V_{oc}}\right)^2 - \frac{1}{r_c^2}}}$$


# Short Circuit Test

- **Short circuit test** is to determine the parameters of the windings  $x_e, r_e$ .
- **LV side is short-circuited**. A reduced voltage is applied to HV side to reach rated current flows.
- Current, voltage, and power at HV side are measured.
- In such a case, the magnetizing branch can be neglected since the magnetizing current is negligible compared to the rated current.
- The watt-meter shows the winding loss.

$$r_e = \frac{P_{sc}}{I_{sc}^2}$$

- The magnitude of the winding impedance is

$$\|r_e + jx_e\| = \frac{V_{sc}}{I_{sc}} \rightarrow x_e = \sqrt{\left(\frac{V_{sc}}{I_{sc}}\right)^2 - r_e^2}$$

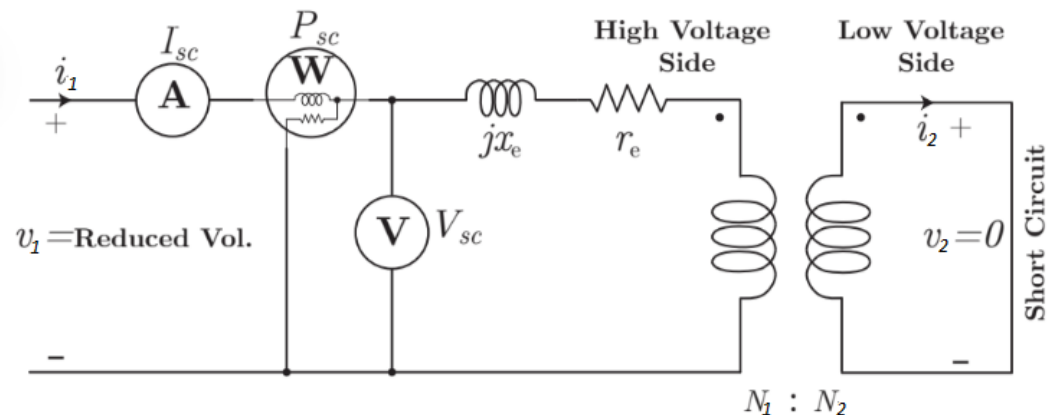

## Example 4 – Transformer Parameter Calculation

These data were obtained when open-circuit and short circuit tests were conducted on a single-phase transformer with the power rating of 50kVA with the rated frequency of 60 Hz. The rated voltages of the high-voltage and low-voltage sides are 2400 V and 240 V, respectively.

	Voltage (V)	Current (A)	Power (W)
HV Winding O/C	240	4.85	180
LV Winding S/C	50	20.8	600

Calculate the equivalent circuit of the transformer referred to the low voltage side.

### Solution

Using the open-circuit test data,  $r_c$  and  $x_m$  can be calculated:

$$r_c = \frac{V_{oc}^2}{P_{oc}} = \frac{240^2}{180} = 320\Omega$$

$$x_m = \frac{1}{\sqrt{\left(\frac{I_0}{V_{oc}}\right)^2 - \frac{1}{r_c^2}}} = \frac{1}{\sqrt{\frac{4.85^2}{240^2} - \frac{1}{320^2}}} = 50.08\Omega$$

## Example 4 – Transformer Parameter Calculation

Using the short-circuit test data,  $r_e$  and  $x_m$  can be calculated:


$$r_e = \frac{P_{sc}}{I_{sc}^2} = \frac{600}{20.8^2} = 1.38\Omega$$

$$x_e = \sqrt{\left(\frac{V_{sc}}{I_{sc}}\right)^2 - r_e^2} = \sqrt{\left(\frac{50}{20.8}\right)^2 - 1.38^2} = 1.96\Omega$$

It must be noted that  $x_e$  and  $r_e$  are at HV side. Since the equivalent model at LV side is asked,  $x_e$  and  $r_e$  must be referred to the low voltage side.


$$d = \frac{N_2}{N_1} = \frac{V_{low}}{V_{high}} = \frac{240}{2400} = 0.1$$
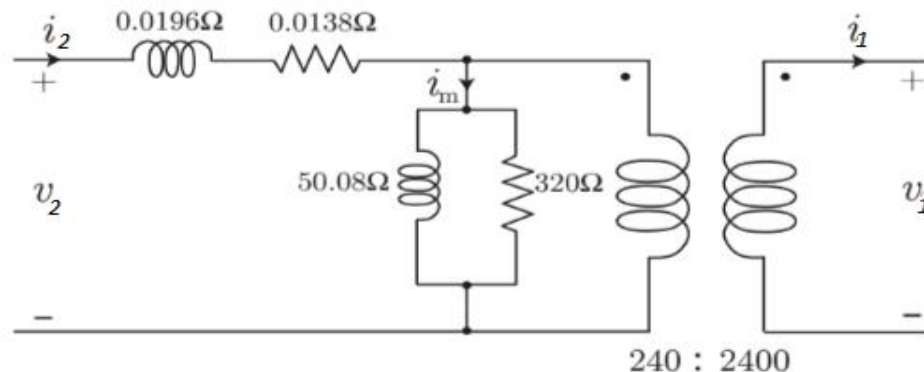
$$r'_e = d^2 \times r_e = 0.1^2 \times r_e = 0.0138\Omega \quad x'_e = d^2 \times x_e = 0.1^2 \times x_e = 0.0196\Omega$$





# Vector Group Notation

	<b>Dd0</b>		<b>Dd6</b>
	<b>Yy0</b>		<b>Yy6</b>
	<b>Dz0</b>		<b>Dz6</b>
	<b>Dy11</b>		<b>Dy5</b>
	<b>Yd11</b>		<b>Yd5</b>
	<b>Yz11</b>		<b>Yz5</b>

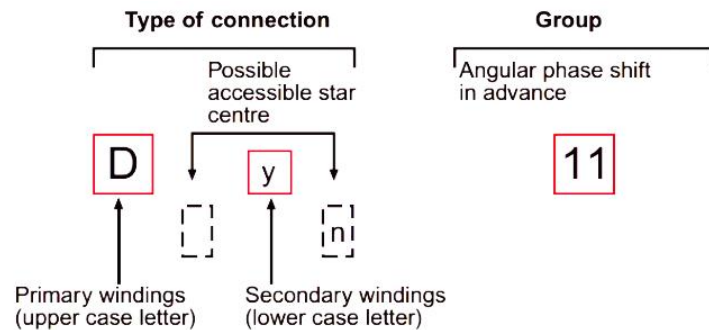

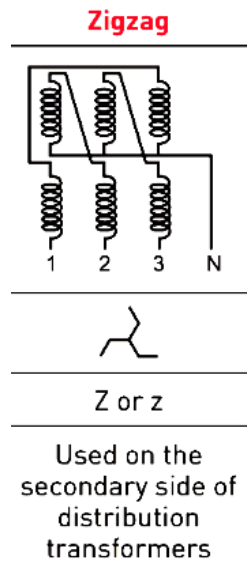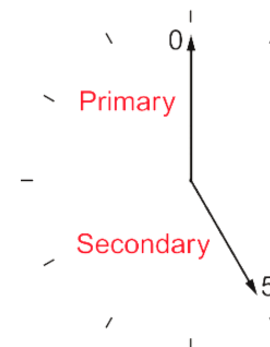- **Y** – star connection
- **D** – delta connection
- **Z** – zigzag connection





# Y – Y Connection

The turns ratio of the transformer is  $N_1/N_2$ , while the line-to-line voltage ratio of the transformer is  $V_{ab}/V_{AB}$ .

$$\frac{N_1}{N_2} = \frac{V_{an}}{V_{AN}} = \frac{\sqrt{3}V_{an}}{\sqrt{3}V_{AN}} = \frac{V_{ab}}{V_{AB}}$$


The current ratio is the inverse of the turn ratio.

$$\frac{N_1}{N_2} = \frac{I_A}{I_a}$$

Y-Y connections are common in transmission systems.
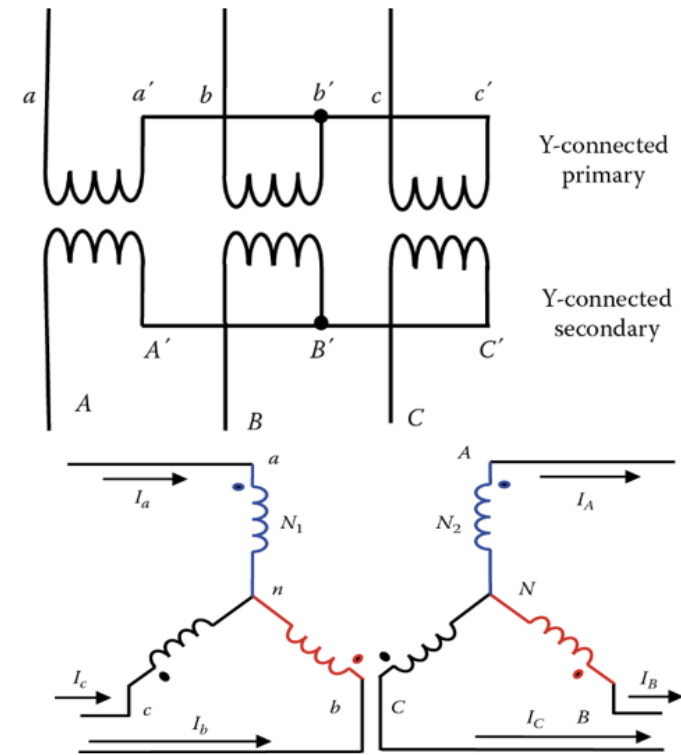
## Advantages

- ability to ground each side
- no phase shift introduced



# Delta-Delta Connection

- Currents in transformer windings are phase current
- Currents in lines feeding the transformers are line current.

Turns ratio of transformer is  $N_1/N_2$

Voltage ratio of transformer is ratio of voltages  $V_{ab}/V_{AB}$ , which are the same as the ratio of the line-to-line voltages in the delta configuration.

Keep in mind that the voltage per turn is constant in any winding. Hence,

$$V_T = \frac{V_{ab}}{N_1} = \frac{V_{AB}}{N_2}$$


$$\frac{N_1}{N_2} = \frac{V_{ab}}{V_{AB}}$$

Using the magnetomotive force equation, we can compute the current ratio

$$\mathfrak{F} = I_{ab}N_1 = I_{AB}N_2$$

$$\frac{N_1}{N_2} = \frac{I_{AB}}{I_{ab}}$$

- Disadvantage: Cannot be grounded.

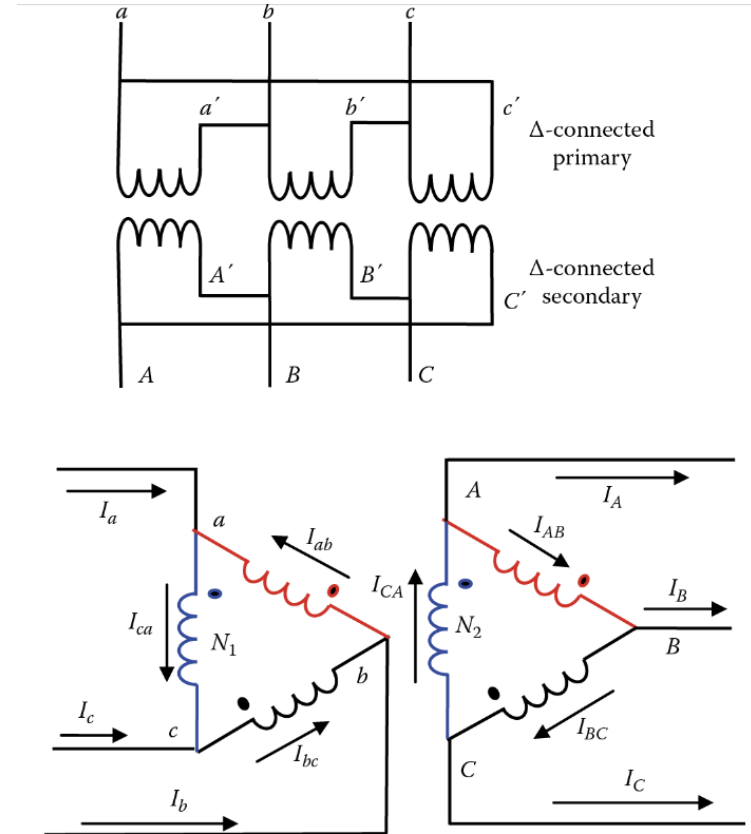

# Delta-Wye Connection

Voltage across  $N_1$  is the phase voltage of the primary circuit  $V_{an}$  and voltage across  $N_2$  is line-to-line voltage of secondary circuit  $V_{AB}$ . Since voltage turns ratio as

$$V_T = \frac{V_{an}}{N_1} = \frac{V_{AB}}{N_2}$$

$$\frac{N_1}{N_2} = \frac{V_{an}}{V_{AB}}$$


$$\frac{N_1}{N_2} = \frac{I_{AB}}{I_a}$$

Similarly, current through  $N_1$  is line current of primary circuit  $I_a$  and current through  $N_2$  is phase current of the secondary winding  $I_{AB}$ .

Hence, we can compute the current ratio using the ampere-turn equation.

$$\mathfrak{F} = I_a N_1 = I_{AB} N_2$$

$$\frac{N_1}{N_2} = \frac{I_{AB}}{I_a}$$

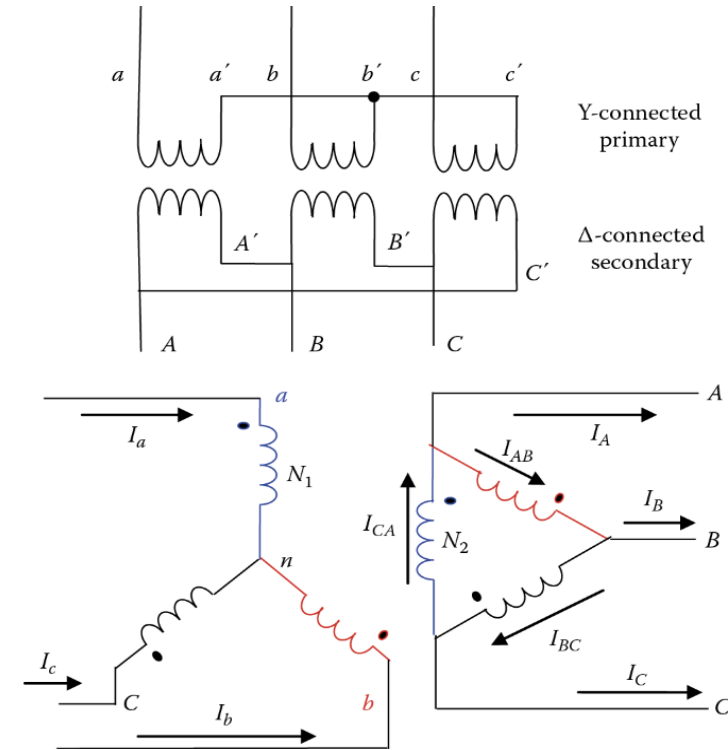

# $\Delta$ - Y Connection: V/I Relationships

## Voltage Relationship

$$V_{AB} = \sqrt{3}V_{An}\angle 30^\circ$$

$$V_{AB} = a \cdot V_{an}$$


$$V_{an} = \frac{\sqrt{3}V_{An} \cdot \angle 30^\circ}{a}$$

## Current Relationship

$$\frac{I_{AB}}{I_a} = \frac{1}{a} \rightarrow I_a = a I_{AB}$$

$$I_A = \sqrt{3}I_{AB}\angle -30^\circ \rightarrow I_{AB} = \frac{1}{\sqrt{3}}I_A\angle 30^\circ$$
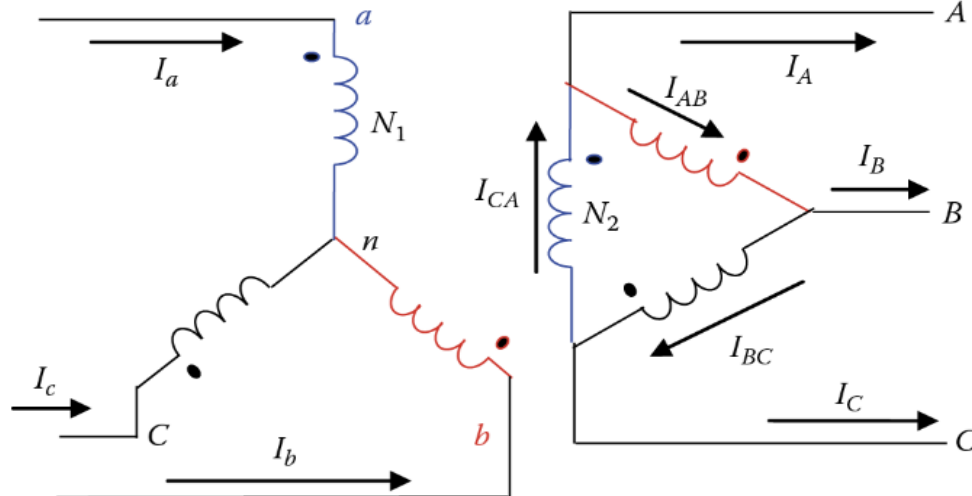
$$I_a = a \frac{1}{\sqrt{3}}I_A\angle 30^\circ$$



## Example 5 – Parameters in Delta-Wye Transformer

A 25kVA transformer has a voltage ratio of 20kV(Y)/10kV(Δ). Compute the following:

1. Winding voltages
2. Turns ratio
3. Line currents in the primary and secondary circuits
4. Phase currents of the transformer

### Solution

1. Winding Voltage

The primary windings of the transformer are connected in wye. Hence, the voltage across the winding is

$$V_{an} = \frac{V_{ab}}{\sqrt{3}} = \frac{20}{\sqrt{3}} = 11.55\text{kV}$$

The secondary windings are connected in delta. Hence, the winding voltage is equal to the line-to-line voltage

$$V_{AB} = 10\text{kV}$$

## Example 5 – Parameters in Delta-Wye Transformer

### 2. Turn Ratio

The turns ratio is the ratio of the voltages of the windings

$$\frac{N_1}{N_2} = \frac{11.55}{10} = 1.155$$

### 3. Line Current in HV and LV sides

$$I_a = \frac{S}{\sqrt{3}V_{ab}} = \frac{25}{\sqrt{3} \times 20} = 0.7217 \text{ A}$$

$$I_A = \frac{S}{\sqrt{3}V_{AB}} = \frac{25}{\sqrt{3} \times 10} = 1.4434 \text{ A}$$

### 4. Phase currents of the transformer


Since the primary windings are connected in wye, the phase current of the primary winding is the same as the line current of the primary circuit.

The secondary windings are connected in delta, hence the phase current of the secondary winding is

$$I_{AB} = \frac{I_A}{\sqrt{3}} = \frac{1.4434}{\sqrt{3}} = 0.8333 \text{ A}$$
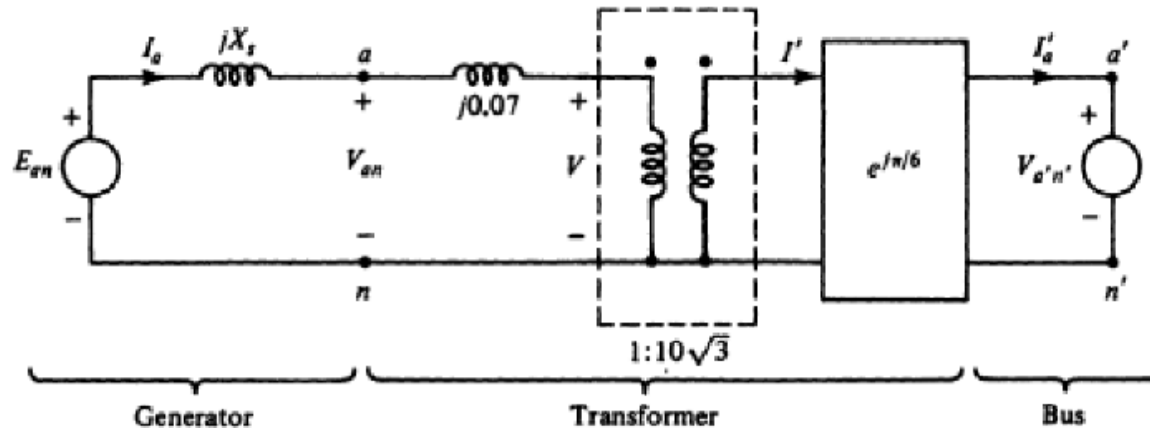
## Example 6 – Parameters in Delta-Wye Transformer

Generator with  $\Delta$ -Y step up transformer. Transformer is made of identical 1 $\phi$  transformers with  $X_1 = 0.21\Omega$ ,  $n = N_1/N_2 = 10$ . Each generator phase is modeled as a Thevenin equivalent circuit. The transformer delivers 100MW at 0.9 lagging power factor at 230kV to the bus.



Find the primary current, primary voltage LL, and 3 $\phi$  complex power supplied by the generator.

### Solution

$$V_{a'n'} = 230/\sqrt{3} \angle 0^\circ \text{ kV} = 132.8 \angle 0^\circ \text{ kV}$$

$$S' = \frac{100 \times 10^6}{0.9 \times 3} \angle 25.84^\circ = 37.04 \angle 25.84^\circ \text{ MVA}$$

$$I'_a = \left( \frac{S'}{V_{a'n'}} \right)^* = \left( \frac{37.04 \angle 25.84^\circ}{132.8 \angle 0^\circ} \right)^* = 278.9 \angle -25.84^\circ$$

## Example 6 – Parameters in Delta-Wye Transformer

By current conversion factor,


$$I_a = 10\sqrt{3}\angle -30^\circ \quad I'_a = 4830.6\angle -55.84^\circ$$

$$\begin{aligned} V_{an} &= V + j0.071I_a \\ &= \frac{1}{10\sqrt{3}} 132.8 \times 10^3 \angle -30^\circ + j0.07 \times 4830.6 \angle 55.84^\circ \\ &= 7667.2 \angle -30^\circ + 338.1 \angle 34.16^\circ \\ &= 7820.5 \angle -27.77^\circ \text{V} \end{aligned}$$

$$V_{ab} = \sqrt{3} \angle -30^\circ V_{an} = 13.55 \angle -57.77^\circ \text{kV}$$

$$S_{1\phi} = V_{an} I_a^* = 37.77 \angle 28.07^\circ \text{MVA}$$
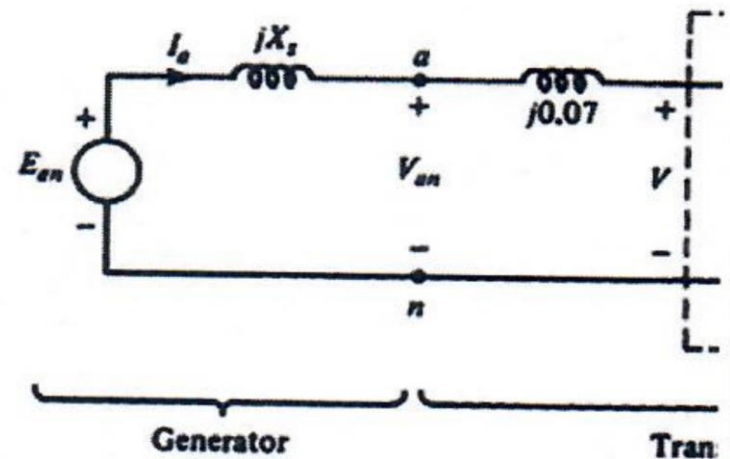
$$S_{3\phi} = 3S = 113.33 \angle 28.07^\circ \text{MVA}$$





# Transformer Efficiency and Voltage Regulation

**Transformer Efficiency** is given by

$$\begin{aligned}\eta &= \frac{P_o}{P_{in}} = \frac{\text{Output power}}{\text{Input power}} = \frac{\text{Output power}}{\text{Output power} + \text{Losses}} \\ &= \frac{V_2' I_2' \cos \theta_2}{V_2' I_2' \cos \theta_2 + P_{cu} + P_{Fe}} \times 100\%.\end{aligned}$$

The losses of the transformer are due to  $R_1$ ,  $R_2$ , and  $R_o$ . The losses in  $R_1$  and  $R_2$  are copper losses  $P_{cu}$  (the windings are made of copper material). The loss in  $R_o$  is known as iron loss  $P_{Fe}$  (the core is made of iron).

**Voltage regulation of transformer** indicates the voltage reduction due to various parameters of the transformer.

$$\varepsilon = \frac{|V_{no\ load}| - |V_{full\ load}|}{|V_{full\ load}|}$$

$|V_{no\ load}|$  is magnitude of **open circuit voltage** measured at the load terminals

$|V_{full\ load}|$  is magnitude of voltage at load terminals when **rated current** is delivered to the load

At no load, (open circuit)  $I_2 = 0$ ,  $V_{no\ load} = V_1$ ,  $V_{full\ load} = V_2'$

$$\varepsilon = \frac{V_1 - aV_2}{aV_2} * 100\%, \text{ where } a = \frac{N_1}{N_2}$$

# Per Unit Calculation

## Motivation

It would be difficult to continuously refer impedance to the different sides of transformer.

Mathematically,

$$\text{Quantity in Per Unit} = \frac{\text{Actual Quantity}}{\text{Base value of the Quantity}}$$

For **Single Phase System**,

Pick base power  $S_B$  [MVA] and voltage base  $V_B$  [kV].

Calculate current base  $I_B$  and Impedance base  $Z_B$ .

$$S_B = V_B \cdot I_B^*$$

$$I_B = \left( \frac{S_B}{V_B} \right)^* = \frac{S_B}{V_B}$$


$$Z_B = \frac{(V_B)^2}{S_B}$$

[Note: Base values are real numbers]

$S_B$  is for the entire system.

$V_B$  is for each different voltage level.

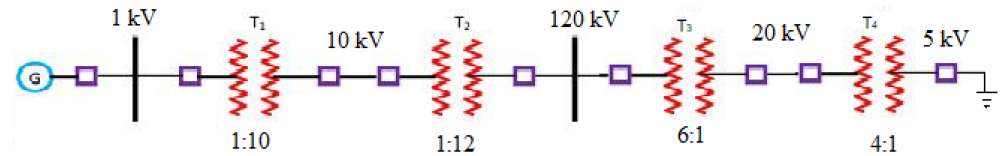Base voltages are related by transformer turns ratio.




# Per Unit Calculation

- Per Unit Values of Primary and Secondary Side of a transformer are **EQUAL**.

$$\begin{array}{cc}
 a = \frac{N_1}{N_2} & V_2 = n \cdot V_1 = \frac{V_1}{a} \\
 n = \frac{N_2}{N_1} & I_2 = \frac{I_1}{n} = a \cdot I_1
 \end{array}$$

Transformation Ratio
Real Values
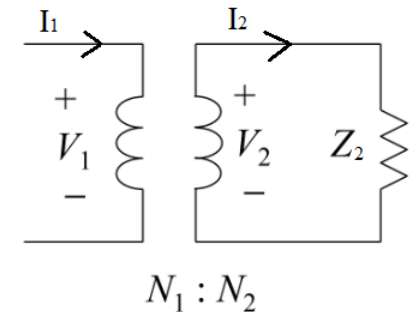
$$\begin{array}{ll}
 V_{p.u} = \frac{V}{V_B} & P_{p.u} = \frac{P}{S_B} \\
 S_{p.u} = \frac{S}{S_B} & Q_{p.u} = \frac{Q}{S_B} \\
 I_{p.u} = \frac{I}{I_B} & R_{p.u} = \frac{R}{Z_B} \\
 Z_{p.u} = \frac{Z}{Z_B} & X_{p.u} = \frac{X}{Z_B}
 \end{array}$$



Choose Base Values

$S_B$

$V_{1B}$  &  $V_{2B} = \frac{V_{1B}}{a} = nV_{1B}$

Per Unit Voltage:

$$V_{2,pu} = \frac{V_2}{V_{2B}} = \frac{n \cdot V_1}{n \cdot V_{1B}} = \frac{V_1}{V_{1B}} = V_{1,pu}$$

Per Unit Current:

$$I_{2,pu} = \frac{I_2}{I_{2B}} = \frac{I_2}{\frac{S_B}{V_{2B}}} = \frac{V_{2B} \cdot I_2}{S_B} = \frac{n \cdot V_{1B} \cdot I_2}{S_B} = \frac{n \cdot V_{1B} \cdot a \cdot I_1}{S_B} = \frac{V_{1B} \cdot I_1}{S_B} = \frac{I_1}{\frac{S_B}{V_{1B}}} = \frac{I_1}{I_{1B}} = I_{1,pu}$$

# Per Unit Calculation

- Per Unit Values of Primary and Secondary Side of a transformer are **EQUAL**.

Voltage: 
$$V_{2,pu} = \frac{V_2}{V_{2B}} = \frac{n \cdot V_1}{n \cdot V_{1B}} = \frac{V_1}{V_{1B}} = V_{1,pu}$$


Current: 
$$I_{2,pu} = \frac{I_2}{I_{2B}} = \frac{I_2}{\frac{S_B}{V_{2B}}} = \frac{V_{2B} \cdot I_2}{S_B} = \frac{n \cdot V_{1B} \cdot I_2}{S_B} = \frac{n \cdot V_{1B} \cdot a \cdot I_1}{S_B} = \frac{V_{1B} \cdot I_1}{S_B} = \frac{I_1}{\frac{S_B}{V_{1B}}} = \frac{I_1}{I_{1B}} = I_{1,pu}$$

Impedance: 
$$Z_{2B} = \frac{V_{2B}^2}{S_B} = \frac{n^2 \cdot V_{1B}^2}{S_B} = n^2 \cdot Z_{1B}$$
$$Z_{2;p.u} = \frac{Z_2}{Z_{2B}} = \frac{n^2 \cdot z_e}{n^2 \cdot Z_{1B}} = \frac{z_e}{Z_{1B}} = z_{e;p.u.}$$

Under per unit calculation, the primary and secondary quantities through the transformers are the same, hence we don't need to perform any conversion between voltage level.
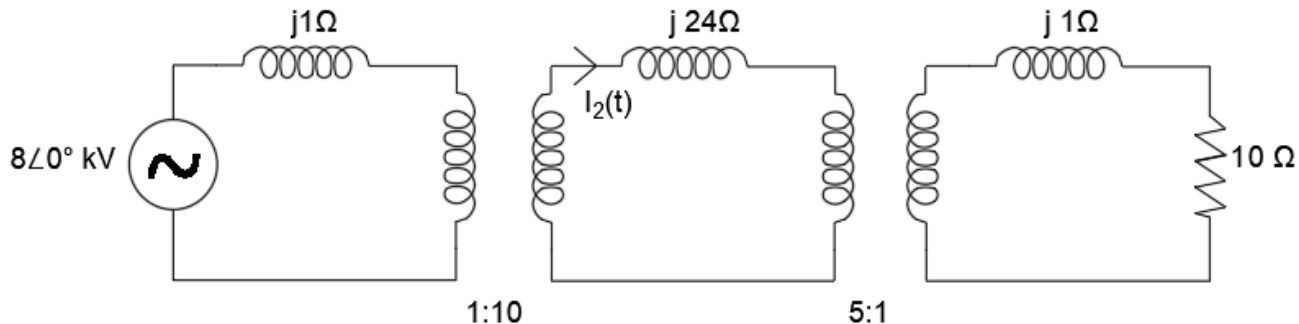
## Example 7: Per Unit Value

Solve for the current, load voltage & load power in the following circuit using P.U. analysis with an  $S_B = 100\text{MVA}$  and base voltage of  $V_{B1} = 8\text{kV}$ ,  $V_{B2} = 80\text{kV}$ , and  $V_{B3} = 16\text{kV}$ .



### Solution

1. Choose Voltage base [kV] and Power base [MVA]

$$V_{B1} = 8\text{kV}; V_{B2} = 80\text{kV}; V_{B3} = 16\text{kV}$$


2. Calculate the impedance base [ $\Omega$ ]

$$Z_{B1} = \frac{(8\text{ kV})^2}{100\text{MVA}} = 0.64\Omega.$$

$$Z_{B2} = \frac{(80\text{ kV})^2}{100\text{MVA}} = 64\Omega.$$

$$Z_{B3} = \frac{(16\text{ kV})^2}{100\text{MVA}} = 2.56\Omega.$$

## Example 7: Per Unit Value

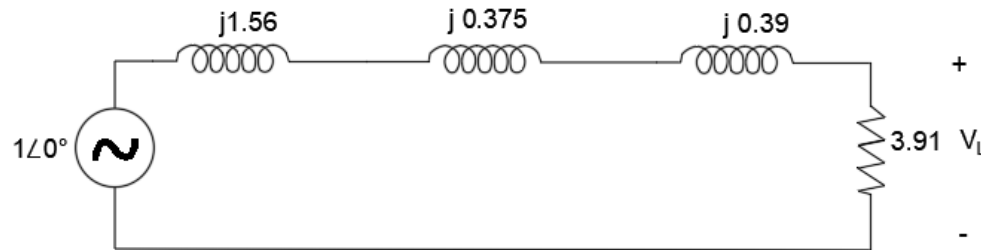

3. Calculate the variables in per unit circuit.

$$I = \frac{1\angle 0^\circ}{3.91 + j2.327} = 0.22\angle -30.8^\circ \text{ p.u.}$$

$$V_L = 1\angle 0^\circ - 0.22\angle(-30.8^\circ) \times j2.327 = 0.859\angle -30.8^\circ \text{ p.u.}$$

$$S_L = V_L \cdot I_L^* = 0.189 \text{ p.u.}$$

$$S_G = V_G \cdot I_G^* = 1\angle 0^\circ \cdot 0.22\angle 30.8^\circ = 0.22\angle 30.8^\circ \text{ p.u.}$$

4. Base Conversion back to Actual Quantities

$$I_{2B} = \frac{100\text{MVA}}{80\text{kV}} = 1250 \text{ A}$$

$$V_L^{\text{actual}} = 0.859\angle(-30.8^\circ) \times 16\text{kV} = 13.7\angle(-30.8^\circ) \text{ kV}$$

$$S_L^{\text{actual}} = 0.189\angle 0^\circ \times 100\text{MVA} = 18.9\angle 0^\circ \text{ MVA}$$

$$S_G^{\text{actual}} = 0.22\angle 30.8^\circ \times 100\text{MVA} = 22\angle 30.8^\circ \text{ MVA}$$

$$I_2^{\text{actual}} = 0.22\angle -30.8^\circ \times 1250 \text{ A} = 275\angle -30.8^\circ \text{ A}$$

# Per Unit Calculation in Three - Phase

- Step 1: Pick a Three-phase **base power** for the entire system  $S_B^{3\phi}$
- Step 2: Pick a **base voltage** for each different voltage level,  $V_{B,LL}$ 
  - L-L Base  $V_{B,LL}$
  - L-N Base  $V_{B,LL}/\sqrt{3}$
- Step 3: Calculate **Base Impedance**

$$Z_B = \frac{\left(\frac{V_{B,LL}}{\sqrt{3}}\right)^2}{\left(\frac{S_B^{3\phi}}{3}\right)} = \frac{V_{B,LL}^2}{S_B^{3\phi}}$$


- Step 4: Calculate **Base current**

$$I_B^{3\phi} = \frac{\frac{S_B^{3\phi}}{3}}{\frac{V_{B,LL}}{\sqrt{3}}} = \frac{S_B^{3\phi}}{\sqrt{3}V_{B,LL}}$$

- Step 5: Convert actual values to p.u.
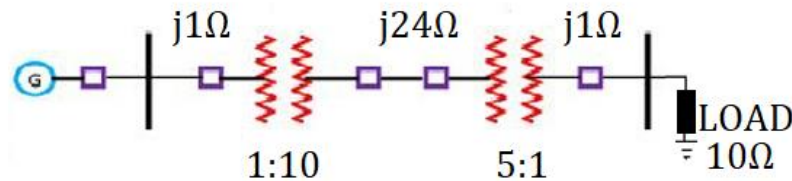
## Example 8 – Per Unit Calculation in 3 Phase


Solve for the current, load voltage and load power in the previous circuit, assuming a 3 $\phi$  base power of 300 MVA, and line to line base voltages of 13.8 kV, 138 kV and 27.6 kV (square root of 3 larger than the 1 $\phi$  example voltages). Also assume the generator is Y-connected so its line-to-line voltage is 13.8 kV.


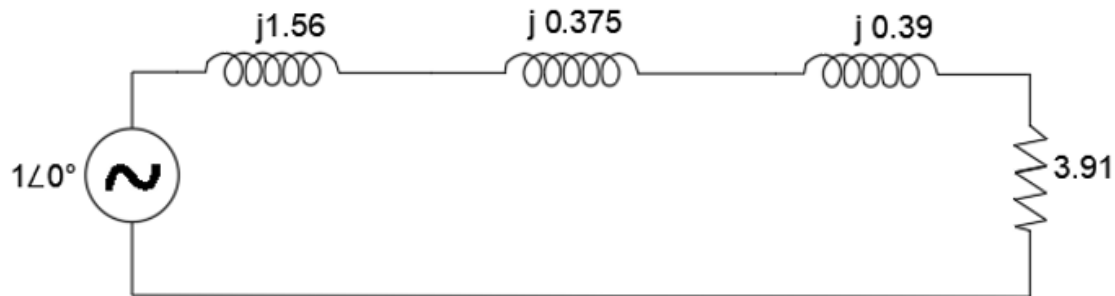
### Solution

Base Voltage:  $V_{B1} = 13.8kV$ ,  $V_{B2} = 138kV$  and  $V_{B3} = 27.6 kV$

Convert the per phase actual circuit into per unit circuit.





## Example 8 – Per Unit Calculation in 3 Phase

- Calculate the variables in per unit circuit.

$$I = \frac{1.0 \angle 0^\circ}{3.91 + j2.327} = 0.22 \angle -30.8^\circ \text{ p.u.}$$

$$V_L = 1.0 \angle 0^\circ - 0.22 \angle -30.8^\circ \times 2.327 \angle 90^\circ = 0.859 \angle -30.8^\circ \text{ p.u.}$$

$$S_L = V_L I_L^* = \frac{|V_L|^2}{Z} = 0.189 \text{ p.u.}$$

$$S_G = 1.0 \angle 0^\circ \times 0.22 \angle 30.8^\circ = 0.22 \angle 30.8^\circ \text{ p.u.}$$

- Convert back to actual value.

$$I_B^{Middle} = \frac{300 \text{ MVA}}{\sqrt{3} (138 \text{ kV})} = 1250 \text{ A}$$

$$V_L^{actual} = 0.859 \angle (-30.8^\circ) \times 27.6 \text{ kV} = 23.8 \angle (-30.8^\circ) \text{ kV}$$


$$S_L^{actual} = 0.189 \angle 0^\circ \times 300 \text{ MVA} = 0.567 \angle 0^\circ \text{ MVA}$$

$$S_G^{actual} = 0.22 \angle 30.8^\circ \times 300 \text{ MVA} = 0.66 \angle 30.8^\circ \text{ MVA}$$

$$I_{Middle}^{actual} = 0.22 \angle -30.8^\circ \times 1250 \text{ A} = 275 \angle -30.8^\circ \text{ A}$$
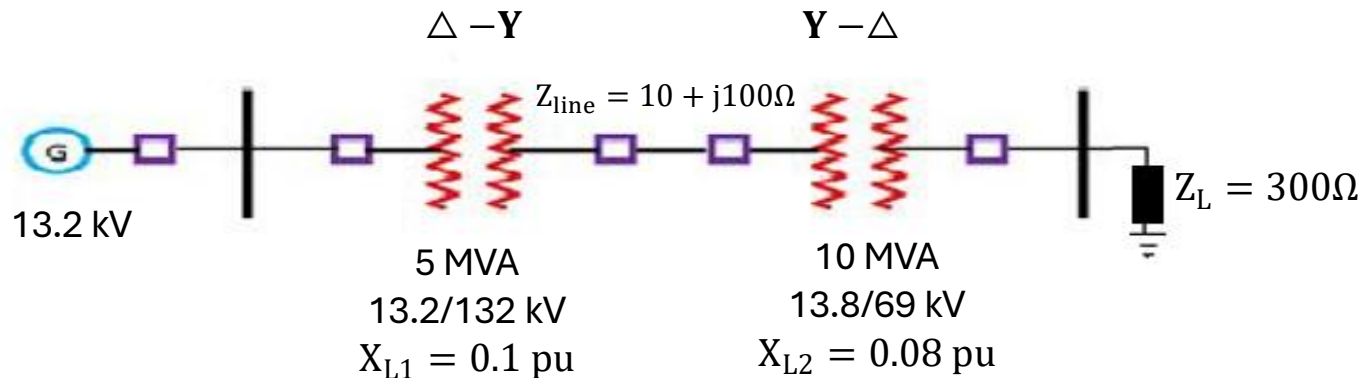
## Example 9 – Base Change

Find the equivalent per unit value for each component.



### Solution

1. Select the power base and voltage base.

$$S_B^{3\phi} = 10 \text{ MVA}$$

$$V_{3B}^{L-L} = 69 \text{ kV} \quad V_{2B}^{L-L} = 138 \text{ kV} \quad V_{1B}^{L-L} = 138 \text{ kV} \times \frac{13.2 \text{ kV}}{132 \text{ kV}} = 13.8 \text{ kV}$$

2. Calculate the impedance base.

$$Z_{3B} = \frac{(V_{3B}^{L-L})^2}{S_B^{3\phi}} = \frac{69^2}{10} = 476\Omega$$

$$Z_{2B} = \frac{(V_{2B}^{L-L})^2}{S_B^{3\phi}} = \frac{138^2}{10} = 1904\Omega$$

$$Z_{1B} = \frac{(V_{1B}^{L-L})^2}{S_B^{3\phi}} = \frac{13.8^2}{10} = 19.04\Omega$$

## Example 9 – Base Change

2. Calculate the impedance base.

$$Z_{\text{load}} = \frac{350\Omega}{476\Omega} = 0.63 \text{ p. u.}$$

$$Z_{\text{line}} = \frac{10 + j100\Omega}{1904\Omega} = 0.005 + j0.05 \text{ p. u.}$$


Calculate also source voltage due to unmatched voltage base.

$$E_s = \frac{13.2\text{kV}}{13.8 \text{ kV}} = 0.96 \text{ p. u.}$$

3. Calculate transformer impedance with base change formula.

$$X_{L2} = \frac{0.08 \times \frac{(V_{3B}^{L-L})^2}{S_B^{3\phi}}}{Z_{3B}} = \frac{0.08 \times \frac{(V_{3B}^{L-L})^2}{S_B^{3\phi}}}{\frac{(V_{3B}^{L-L})^2}{S_B^{3\phi}}} = 0.08$$

$$X_{L1} = \frac{0.1 \times \frac{(13.2\text{kV})^2}{5 \text{ MVA}}}{Z_{1B}} = \frac{0.1 \times \frac{(13.2)^2}{5}}{\frac{(13.8)^2}{10}} = 0.183 \text{ p. u}$$



## **Power System Analysis and Protection**

Karl M.H. LAI

Email: [perspect@connect.hku.hk](mailto:perspect@connect.hku.hk)

Webpage: [Protection Engineer | Karl MH LAI](#)